

# EE230- Analog lab (Homework-4)

## Spring Semester: Year 2021-22

January 29, 2022

---

### Instructions:

- Show your netlists and simulation results of each question to the evaluating TA.
  - **Deadline: Feb 3, 2:00 pm.**
  - **You can refer:** NGSPICE tutorial, model files uploaded on the course moodle / MS Teams channel and your written netlists of previous experiments.
- 

1. Write NGSPICE netlist for the circuit shown in Figure [ 1]. For the given circuit, use a single supply of +5V for the op-amp LM324. Sweep the input voltage ( $V_{in}$ ) from  $0.1V_{dc}$  to  $5V_{dc}$  in the steps of  $0.1V$  and comment on the relationship between  $V_{in}$  and  $V_{out}$ .

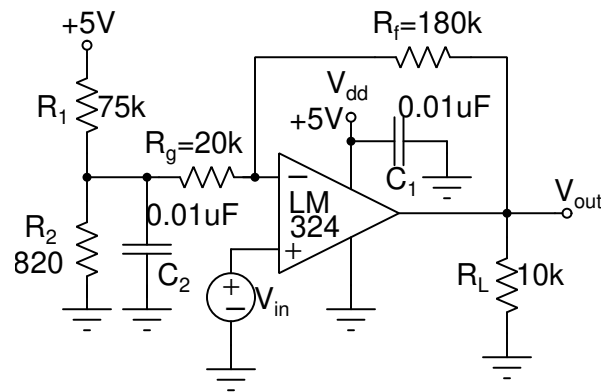


Figure 1: OP-AMP based Circuit-1

2. Write NGSPICE netlist of the circuit shown in Figure [ 2]. Use op-amp 741 and supply voltage of  $\pm 15V$ .

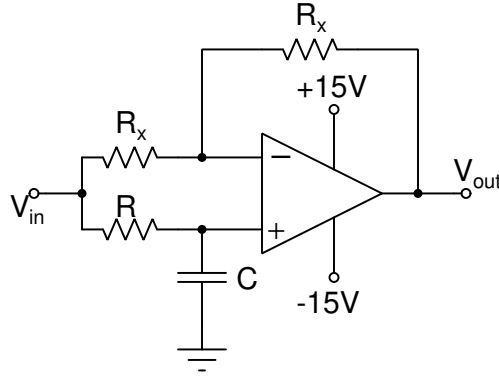


Figure 2: OP-AMP based Circuit-2

- (a) Simulate the circuit, where  $R_x = 10k\Omega$ ,  $R = 10k\Omega$  and  $C = 47nF$ . Perform the AC analysis and observe the phase and gain plots for the circuit. Make sure that the dc component is  $0V$  and ac signal should be  $1V_{pp}$  for the  $V_{in}$  source.
  - (b) Now, repeat above step for  $R_x = 10k\Omega$ ,  $R = 1k\Omega$  and  $C = 1nF$ .
  - (c) Write your observations in the gain plots and phase plots for part (a) and (b)?
  - (d) What is the gain value in linear scale for part (a) and (b)?
  - (e) What is the above circuit called and what are the applications of the circuit you could think of?
3. (a) Write NGSPICE netlist for the circuit shown in Figure [ 3]. Use op-amp 741 and supply voltage of  $\pm 15V$ . In a single window, plot  $V_{out}$  v/s  $V_{in}$  for  $-5V \leq V_{in} \leq +5V$ . Find the values of  $V_{in}$  for which  $V_{out}$  trips.

Upper trip point  $V_T^+ = \text{---}$

Lower trip point  $V_T^- = \text{---}$

- (b) Write NGSPICE netlist for the circuit shown in Figure [ 4]. Use the same op-amp and power supplies as in Part (a). Observe the input and steady state output from 100 ms to 110 ms.
- (c) Write NGSPICE netlist which interconnects the circuits in Figure [ 3] and [ 4] to form a closed loop without any external input.

**Hint:** An output of Figure [ 4] in part (b), let's call it ( $V'_{out}$ ), will be an input to Figure [ 3] in part (a). Also, an output of Figure [ 3] in part (a) will be an input to Figure [ 4] in part (b). **Output of Figure [ 3] will be your final output ( $V_{out}$ ).**

You should re-use the existing netlists from part (a) and (b). **You can use the existing netlists as sub-circuits in writing the netlist for part (c) (optional).**

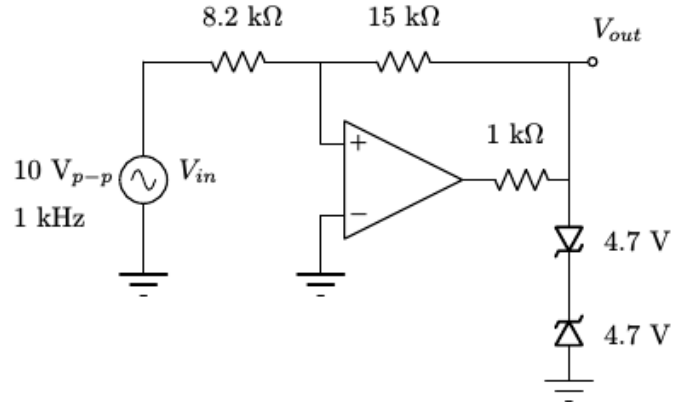


Figure 3: OP-AMP based Circuit-3

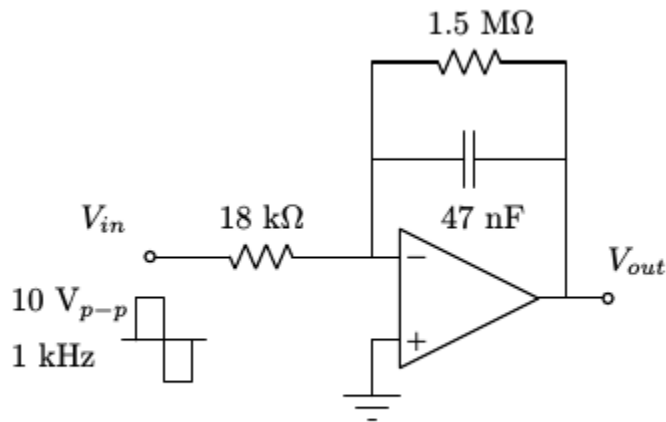


Figure 4: OP-AMP based Circuit-4

- i. Observe the steady state outputs  $V_{out}$  and  $V'_{out}$  from 99 ms to 101 ms.
- ii. Write the frequency of  $V_{out} = \text{---}$

Positive peak of  $V'_{out} = \text{---}$

Negative peak of  $V'_{out} = \text{---}$