

EE230 Homework 1

NGSPICE simulation of RC and RLC circuits

Rohan Rajesh Kalbag, 20D170033

January 12, 2022

1 Overview of the experiment

1.1 Aim of the experiment


To simulate RC Integrator, RC Differentiator, RC lowpass, RC highpass, RC band-pass and RLC bandpass circuits using NGSPICE and realise the circuit diagrams using XCircuit.




1.2 Method



Netlists were made for simulating the circuits in NGSPICE. Xcircuit was used to make the circuit diagrams.

2 Design

2.1 Circuit Diagrams

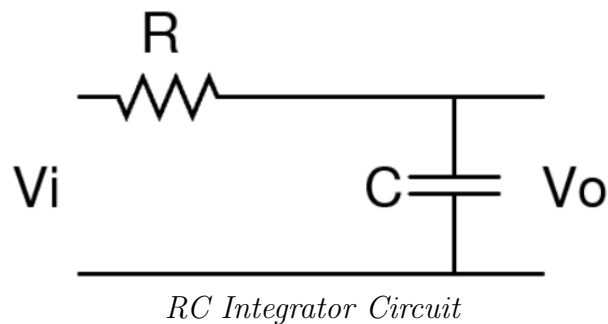

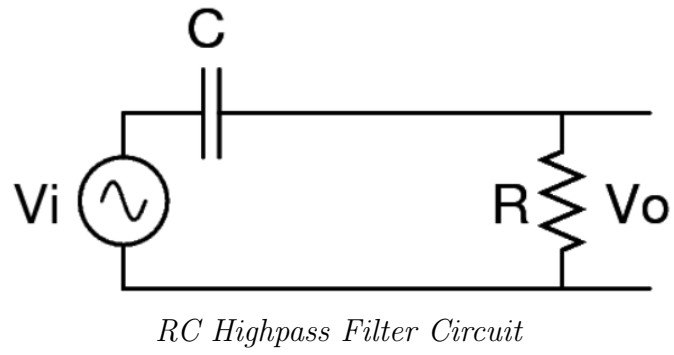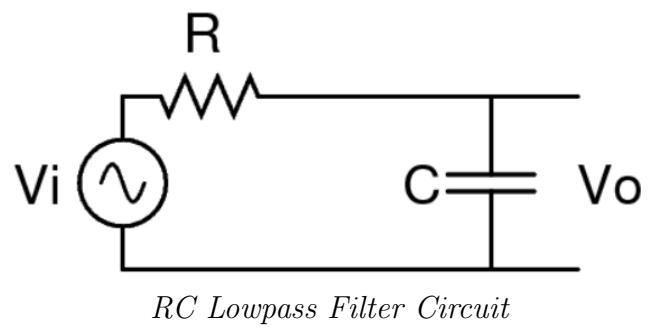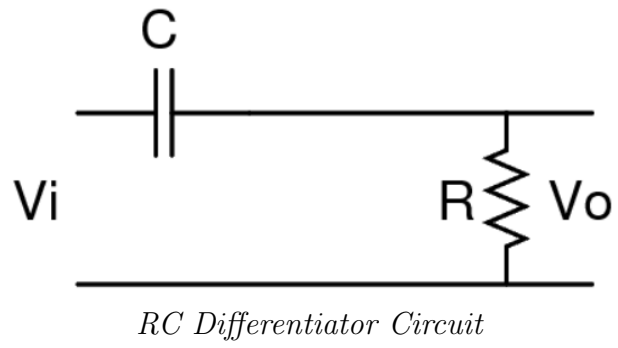

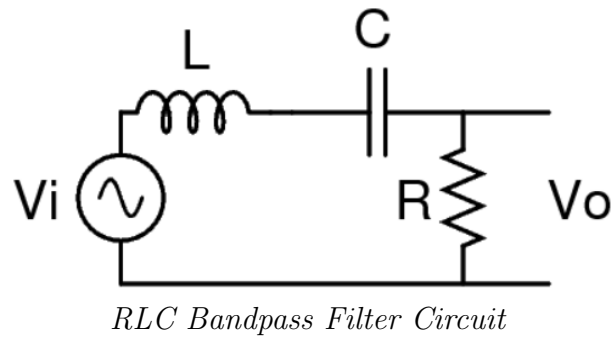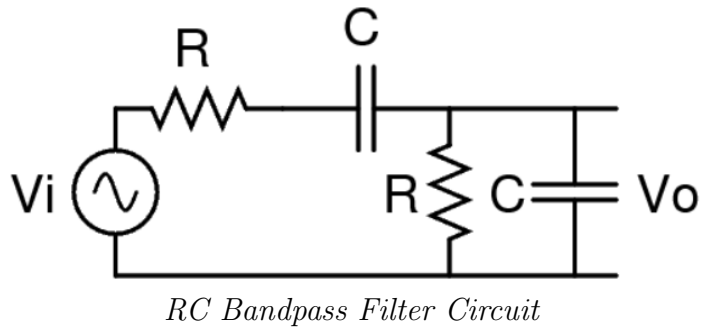

3 Code Snippets

3.1 B1 - RC Integrator

3.1.1 $T = 10\tau$

```

RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.01 0.02)
* Analysis Command
.tran 0.01m 0.06
.control
run
plot v(1) v(2)
.endc
.end

```

3.1.2 $T = 5\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.005 0.01)
* Analysis Command
.tran 0.01m 0.03
.control
run
plot v(1) v(2)
.endc
.end
```

3.1.3 $T = \tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.001 0.002)
* Analysis Command
.tran 0.001m 0.006
.control
run
plot v(1) v(2)
.endc
.end
```

3.1.4 $T = 0.5\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.0005 0.001)
* Analysis Command
.tran 0.001m 0.003
.control
run
plot v(1) v(2)
.endc
.end
```

3.1.5 $T = 0.1\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.0001 0.0002)
* Analysis Command
.tran 0.0001m 0.0006
.control
run
plot v(1) v(2)
.endc
.end
```

3.1.6 $T = 0.05\tau$

RC Integrator

* Components

r1 1 2 10k

c1 2 0 0.1u

V1 1 0 pulse(0 5 0 0 0 0.05m 0.1m)

* Analysis Command

.tran 0.01u 0.3m

.control

run

plot v(1) v(2)

.endc

.end

3.2 B2 - RC Differentiator

3.2.1 $T = 10\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 10m 20m)

* Analysis Command

.tran 0.02m 60m

.control

run

plot v(1) v(2)

.endc

.end

3.2.2 $T = 5\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.005 0.01)

* Analysis Command

.tran 0.002m 0.03

.control

run

plot v(1) v(2)

.endc

.end

3.2.3 $T = \tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.001 0.002)

* Analysis Command

.tran 0.002m 0.006

.control

run

plot v(1) v(2)

.endc

.end

3.2.4 $T = 0.5\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.5m 1m)

* Analysis Command

.tran 0.002m 3m

.control

run

plot v(1) v(2)

.endc

.end

3.2.5 $T = 0.1\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.1m 0.2m)

* Analysis Command

.tran 0.002m 0.6m

.control

run

plot v(1) v(2)

.endc

.end

3.2.6 $T = 0.05\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.05m 0.1m)

* Analysis Command

.tran 0.0001m 0.3m

.control

run

plot v(1) v(2)

.endc

.end

3.3 B3 - RC Lowpass Filter

RC lowpass filter

*Components

r1 1 2 10k

c1 2 0 0.1u

V1 1 0 dc 0 ac 1 \$ac analysis

*Analysis Command

.ac dec 10 1m 100k

.control

run

plot vdb(2)

.endc

.end

3.4 B4 - RC Highpass Filter

```
RC highpass filter
*Components
c1 1 2 0.1u
r1 2 0 10k
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 1m 100k
.control
run
plot vdb(2)
.endc
.end
```


3.5 B5 - RC Bandpass Filter

```
RC bandpass filter
*Components
r1 1 2 10k
c1 2 3 0.1u
r2 3 0 10k
c2 3 0 0.1u
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 500 1m 10Meg
.control
run
plot vdb(3)
print vdb(3)
.endc
.end
```


3.6 B5 - RLC Bandpass Filter

```
RLC bandpass filter
*Components
l1 1 2 10m
c1 2 3 0.1u
r2 3 0 1k
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 500 10m 1000Meg
.control
run
plot vdb(3)
print vdb(3)
.endc
.end
```


3.7 Simulation Plots

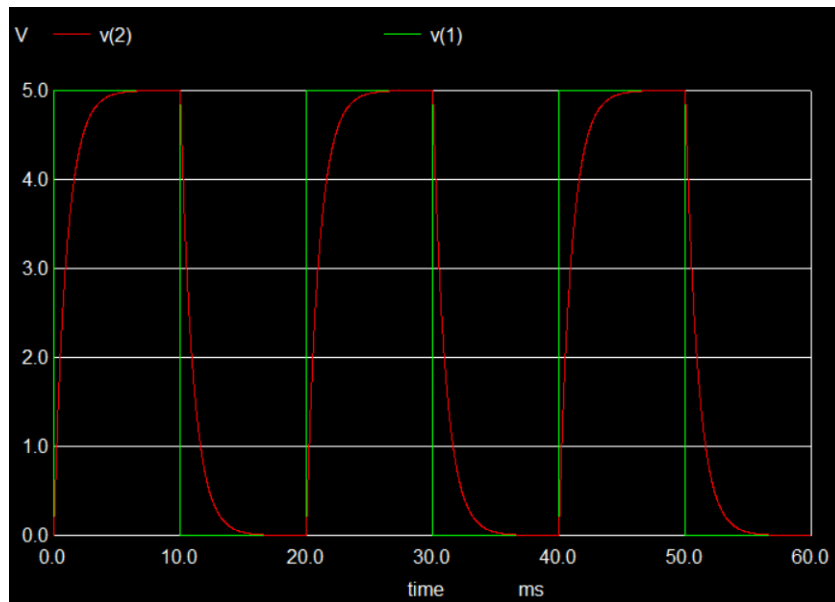

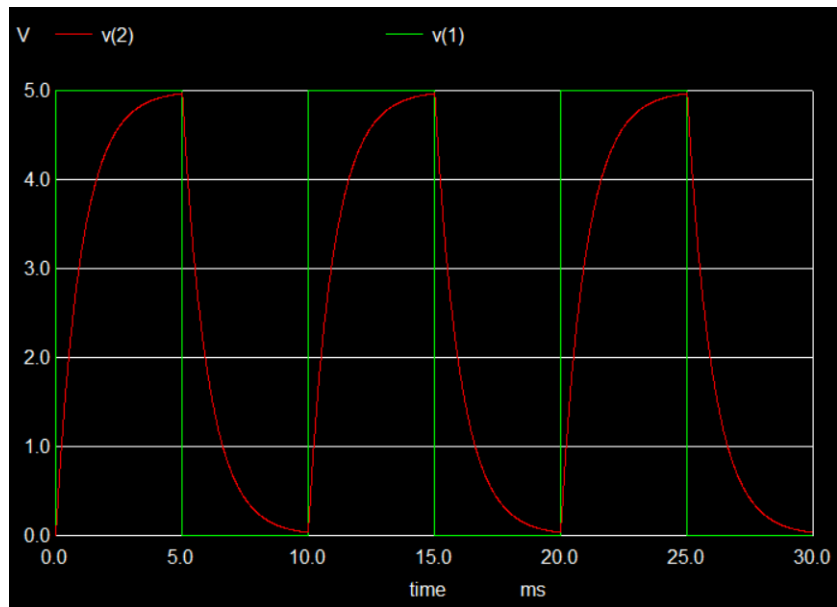
RC Integrator for $T = 10\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



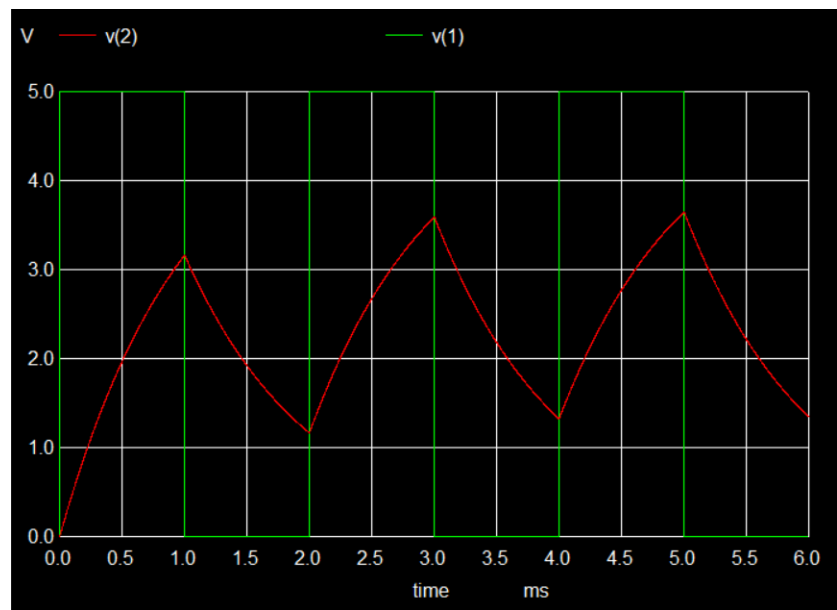
RC Integrator for $T = 5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



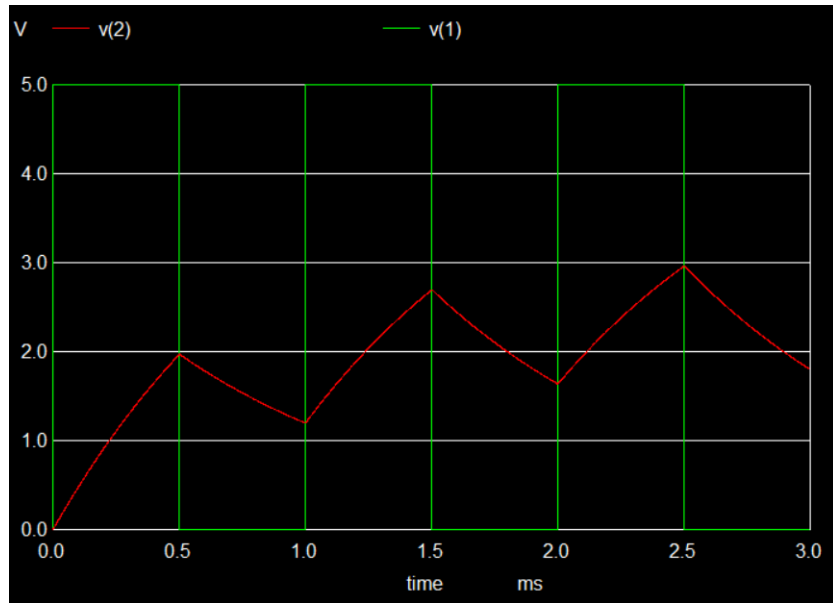
RC Integrator for $T = \tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



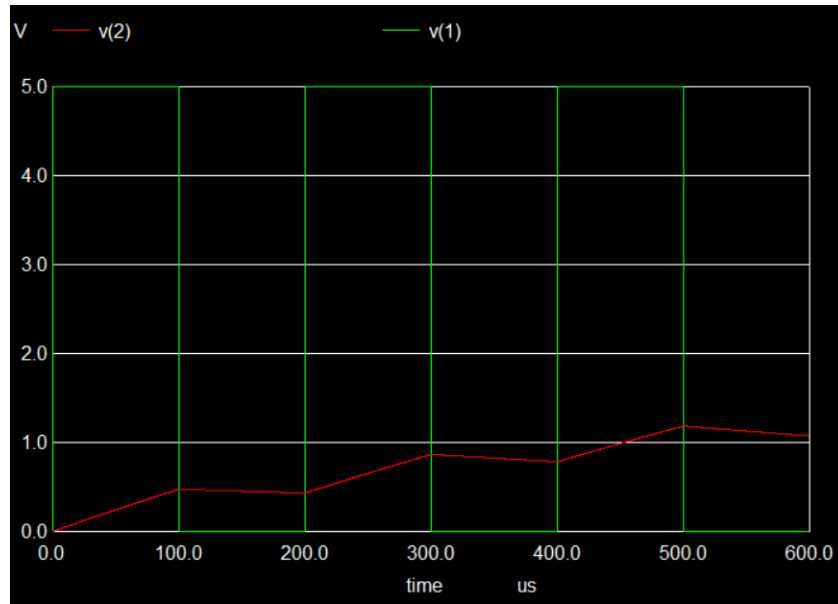
RC Integrator for $T = 0.5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



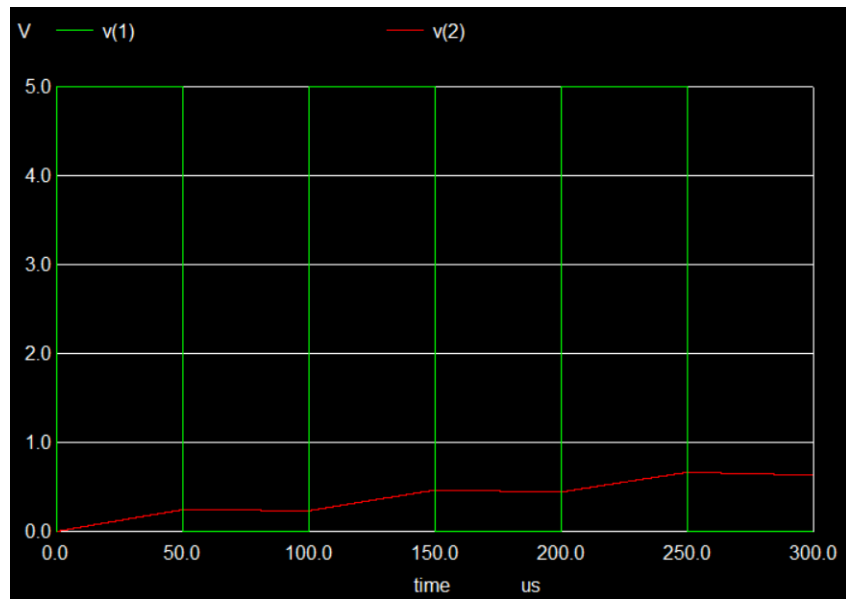
RC Integrator for $T = 0.1\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



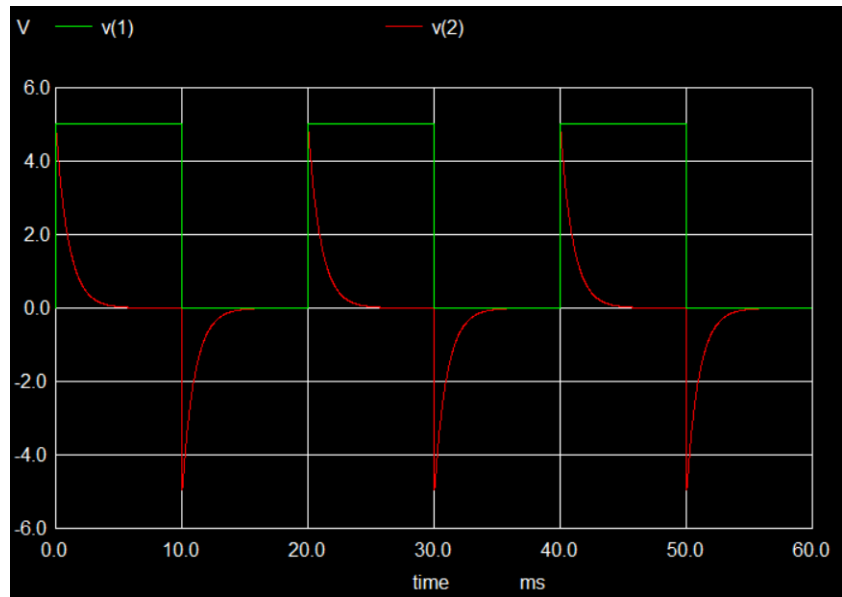
RC Integrator for $T = 0.01\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



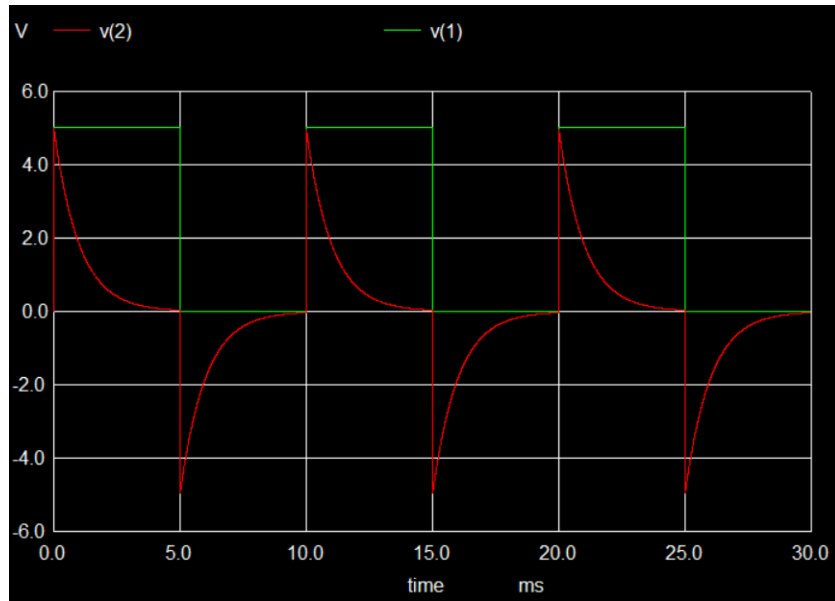
RC Differentiator for $T = 10\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



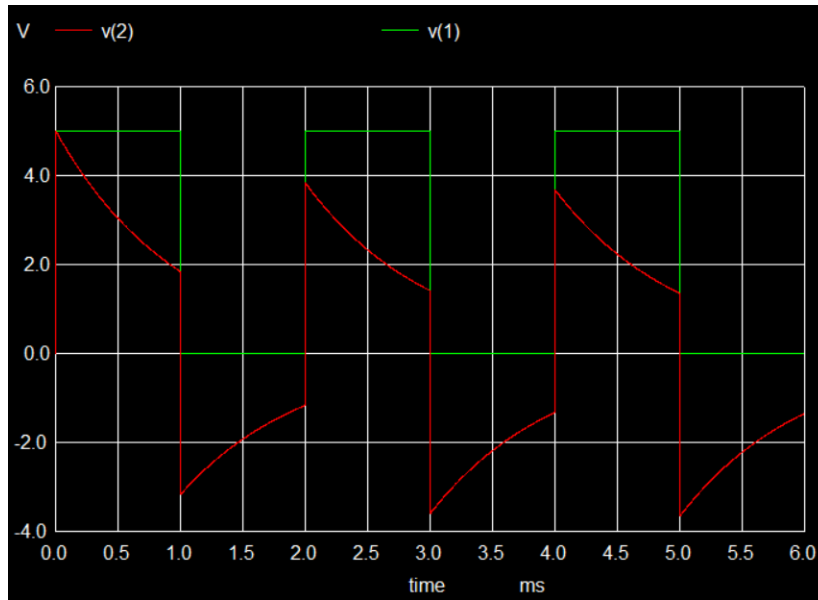
RC Differentiator for $T = 5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



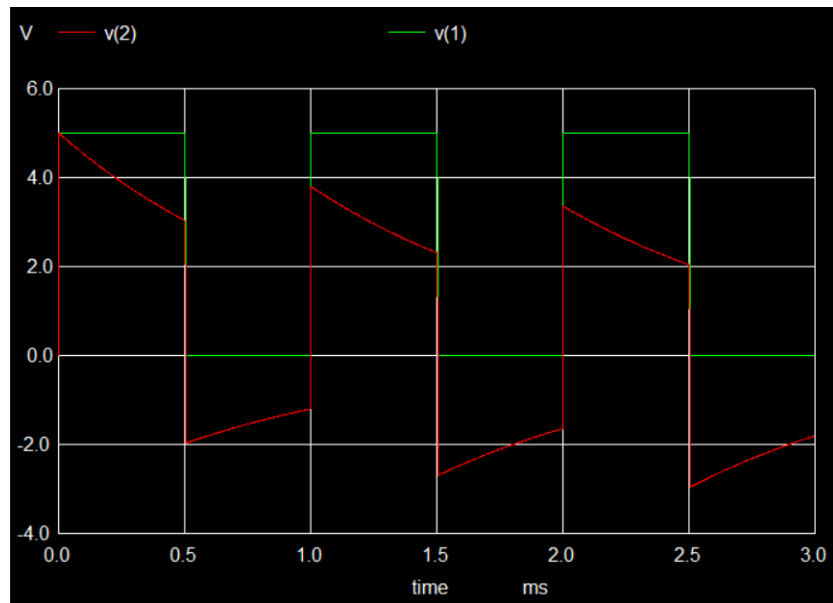
RC Differentiator for $T = \tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



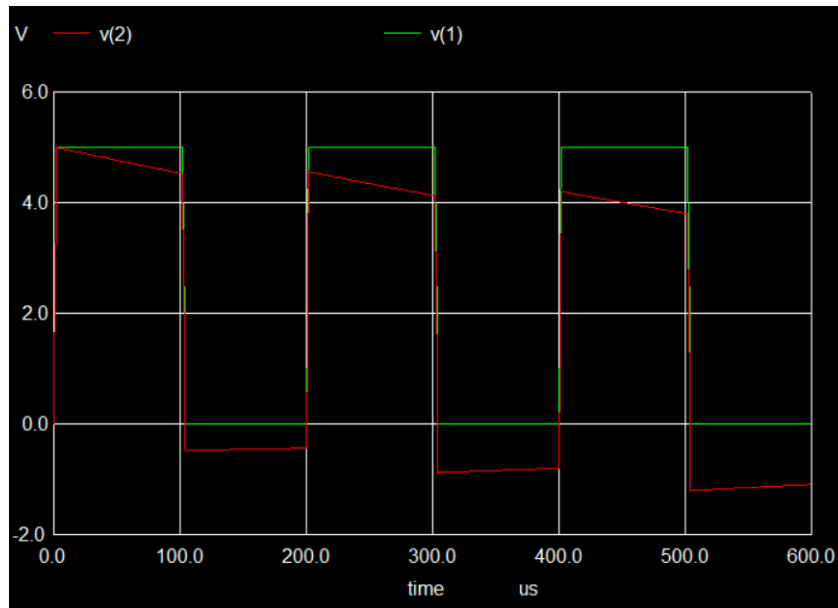
RC Differentiator for $T = 0.5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



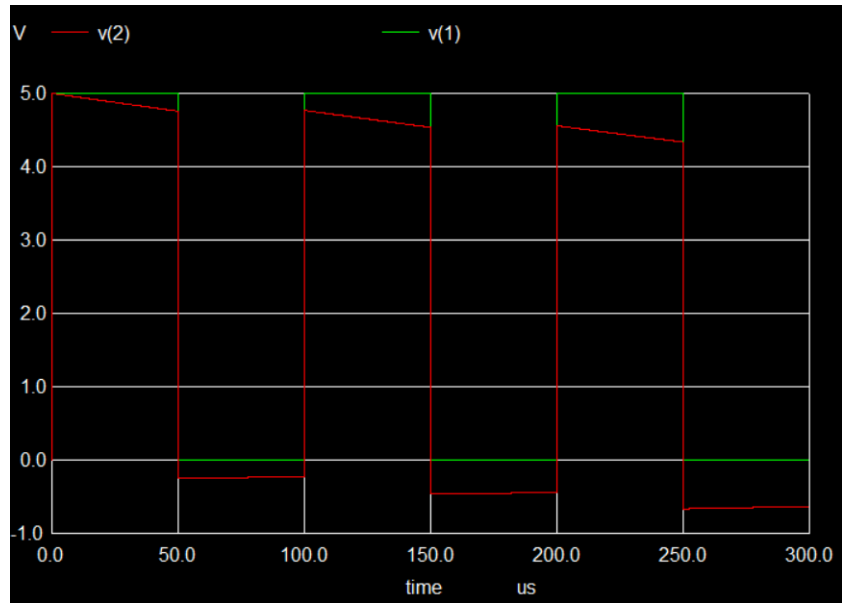
RC Differentiator for $T = 0.1\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



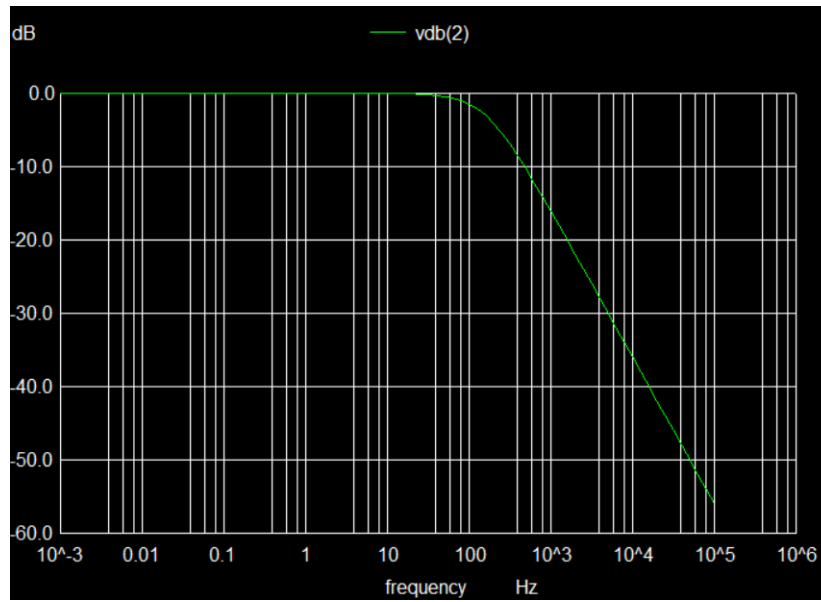
RC Differentiator for $T = 0.01\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}




Amplitude Bode Plot for RC Lowpass Filter
 $vdb(2)$: $20\log_{10}(|V_{out}|)$

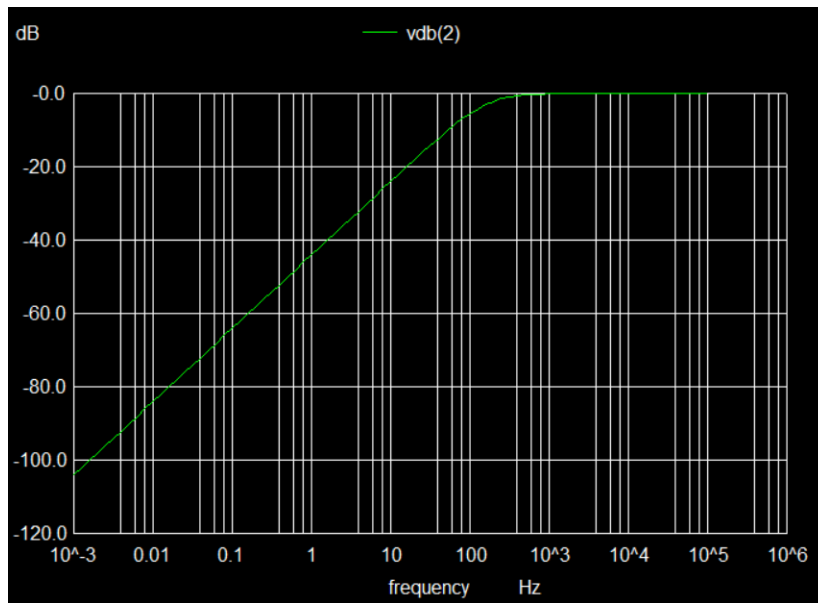

Amplitude Bode Plot for RC Highpass Filter
 $vdb(2): 20\log_{10}(|V_{out}|)$

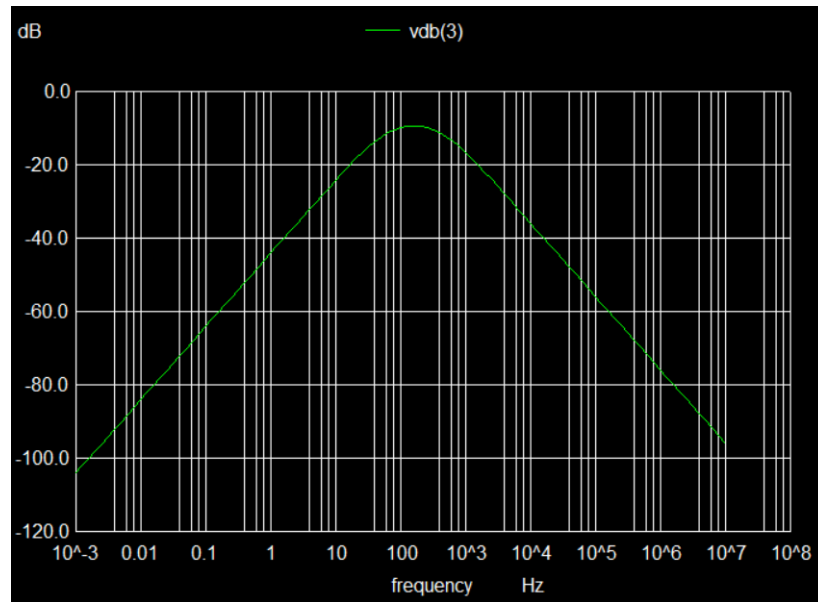

Amplitude Bode Plot for RC Bandpass Filter
 $vdb(3): 20\log_{10}(|V_{out}|)$

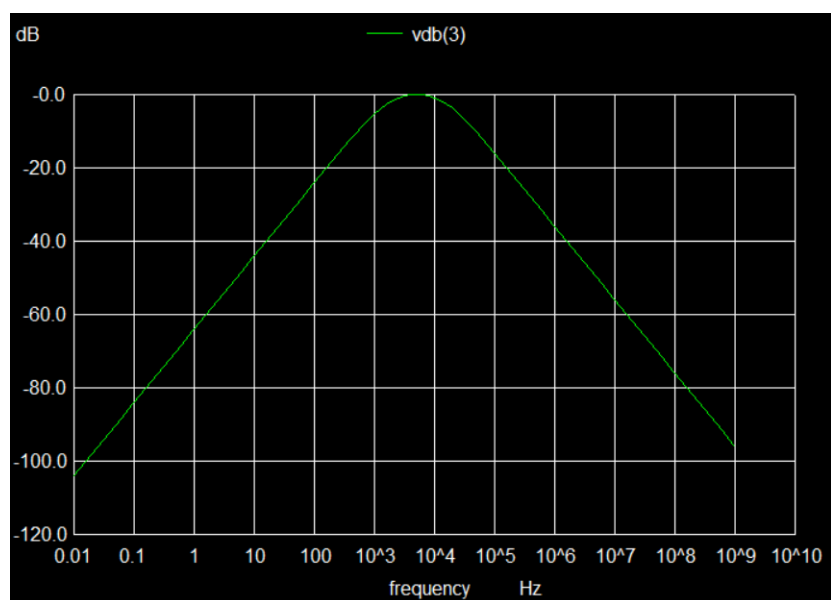

Amplitude Bode Plot for RLC Bandpass Filter
 $vdb(3): 20\log_{10}(|V_{out}|)$

4 Experimental Results

4.1 Parameters obtained for RC and RLC Bandpass filters experimentally

4.1.1 RC Bandpass

Peak Amplitude : -9.542 dB

f_{center} : 159.22 Hz

f_{lower} : 48.30 Hz

f_{upper} : 524.81 Hz

4.1.2 RLC Bandpass

Peak Amplitude : -2.97×10^{-7} dB \approx 0 dB

f_{center} : 5035.01 Hz

f_{lower} : 1465.54 Hz

f_{upper} : 17298.16 Hz

4.2 Parameters obtained for RC and RLC Bandpass filters theoretically

4.2.1 RC Bandpass

Peak Amplitude: $-20\log_{10}(3) = -9.54$ dB

f_{center} : $\frac{1}{2\pi RC} = 159.15$ Hz

f_{lower} : $\frac{(\sqrt{13}-3)}{4\pi RC} = 48.189$ Hz

f_{upper} : $\frac{(\sqrt{13}+3)}{4\pi RC} = 525.65$ Hz

4.2.2 RLC Bandpass

Peak Amplitude: $20\log_{10}(1) = 0$ dB

f_{center} : $\frac{1}{2\pi\sqrt{LC}} = \frac{10^{4.5}}{2\pi} = 5032.93$ Hz

f_{lower} : $(\sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} - \frac{R}{2L}) \cdot \frac{1}{2\pi} = 1457.99$ Hz

f_{upper} : $(\sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} + \frac{R}{2L}) \cdot \frac{1}{2\pi} = 17373.51$ Hz