

EE230 Homework 1

NGSPICE simulation of RC and RLC circuits

Name. Rohan Rajesh Kalbag, Roll. 20D170033



January 12, 2022





1 Overview of the experiment

1.1 Aim of the experiment

To simulate RC Integrator, RC Differentiator, RC lowpass, RC highpass, RC bandpass and RLC bandpass circuits using NGSPICE and realise the circuit diagrams using XCircuit.

1.2 Circuit Diagrams

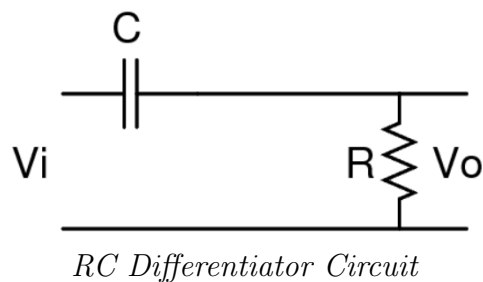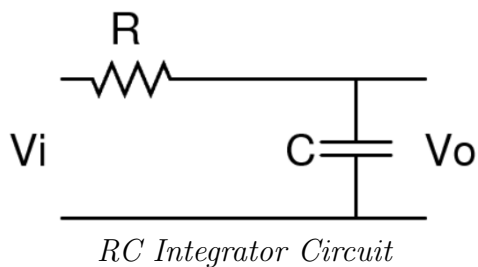

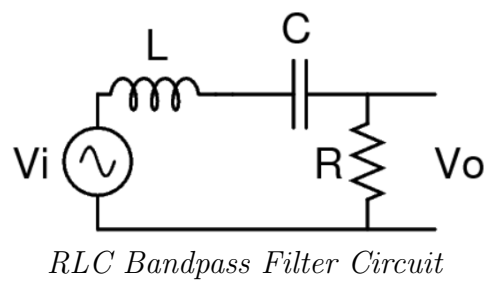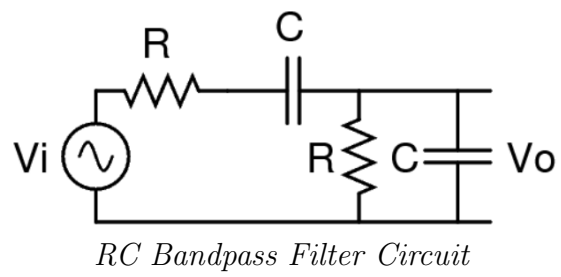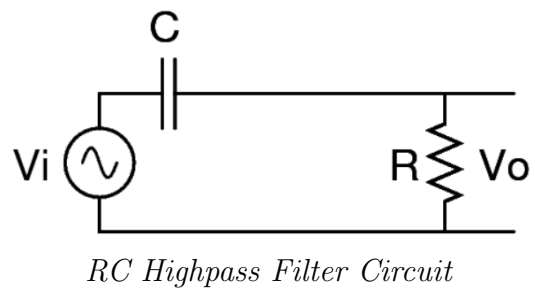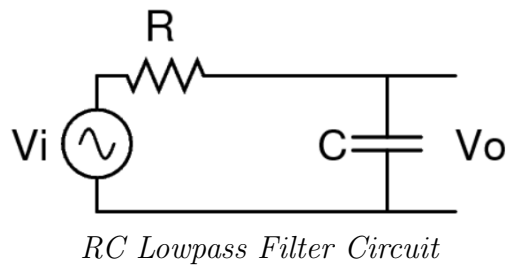

2 Simulation Code Snippets

2.1 B1 - RC Integrator

2.1.1 $T = 10\tau$

RC Integrator

* Components

r1 1 2 10k

c1 2 0 0.1u

V1 1 0 pulse(0 5 0 0 0 0.01 0.02)

* Analysis Command

.tran 0.01m 0.06

.control

run

plot v(1) v(2)

.endc

.end

2.1.2 $T = 5\tau$

RC Integrator

* Components

r1 1 2 10k

c1 2 0 0.1u

V1 1 0 pulse(0 5 0 0 0 0.005 0.01)

* Analysis Command

.tran 0.01m 0.03

.control

run

plot v(1) v(2)

.endc

.end

2.1.3 $T = \tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.001 0.002)
* Analysis Command
.tran 0.001m 0.006
.control
run
plot v(1) v(2)
.endc
.end
```

2.1.4 $T = 0.5\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.0005 0.001)
* Analysis Command
.tran 0.001m 0.003
.control
run
plot v(1) v(2)
.endc
.end
```

2.1.5 $T = 0.1\tau$

RC Integrator

* Components

r1 1 2 10k

c1 2 0 0.1u

V1 1 0 pulse(0 5 0 0 0 0.0001 0.0002)

* Analysis Command

.tran 0.0001m 0.0006

.control

run

plot v(1) v(2)

.endc

.end

2.1.6 $T = 0.05\tau$

RC Integrator

* Components

r1 1 2 10k

c1 2 0 0.1u

V1 1 0 pulse(0 5 0 0 0 0.05m 0.1m)

* Analysis Command

.tran 0.01u 0.3m

.control

run

plot v(1) v(2)

.endc

.end

2.2 B2 - RC Differentiator

2.2.1 $T = 10\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 10m 20m)

* Analysis Command

.tran 0.02m 60m

.control

run

plot v(1) v(2)

.endc

.end

2.2.2 $T = 5\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.005 0.01)

* Analysis Command

.tran 0.002m 0.03

.control

run

plot v(1) v(2)

.endc

.end

2.2.3 $T = \tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.001 0.002)

* Analysis Command

.tran 0.002m 0.006

.control

run

plot v(1) v(2)

.endc

.end

2.2.4 $T = 0.5\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.5m 1m)

* Analysis Command

.tran 0.002m 3m

.control

run

plot v(1) v(2)

.endc

.end

2.2.5 $T = 0.1\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.1m 0.2m)

* Analysis Command

.tran 0.002m 0.6m

.control

run

plot v(1) v(2)

.endc

.end

2.2.6 $T = 0.05\tau$

RC Differentiator

* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.05m 0.1m)

* Analysis Command

.tran 0.0001m 0.3m

.control

run

plot v(1) v(2)

.endc

.end

2.3 B3 - RC Lowpass Filter

```
RC lowpass filter
*Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 1m 100k
.control
run
plot vdb(2)
.endc
.end
```

2.4 B4 - RC Highpass Filter

```
RC highpass filter
*Components
c1 1 2 0.1u
r1 2 0 10k
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 1m 100k
.control
run
plot vdb(2)
.endc
.end
```

2.5 B5 - RC Bandpass Filter

```
RC bandpass filter
*Components
r1 1 2 10k
c1 2 3 0.1u
r2 3 0 10k
c2 3 0 0.1u
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 1m 10Meg
.control
run
plot vdb(3)
print vdb(3)
.endc
.end
```

2.6 B5 - RLC Bandpass Filter

```
RLC bandpass filter
*Components
l1 1 2 10m
c1 2 3 0.1u
r2 3 0 1k
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 10m 1000Meg
.control
run
plot vdb(3)
print vdb(3)
.endc
.end
```

2.7 Parameters obtained for RC and RLC Bandpass filters

2.7.1 RC Bandpass

Peak Amplitude : -9.542 dB

f_{center} : 158.48 Hz

f_{upper} : 630.95 Hz

f_{lower} : 39.810 Hz

2.7.2 RLC Bandpass


Peak Amplitude : -3.05×10^{-5} dB

f_{center} : 5011.872 Hz

f_{upper} : 19952.62 Hz


f_{lower} : 1258.92 Hz

2.8 Simulation Plots

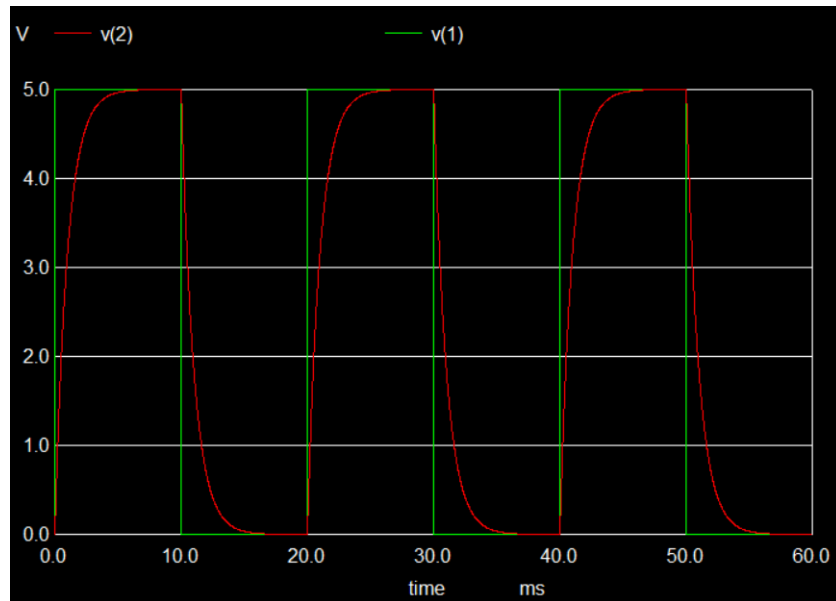


RC Integrator for $T = 10\tau$


$V(1)$: V_{in} , $V(2)$: V_{out}

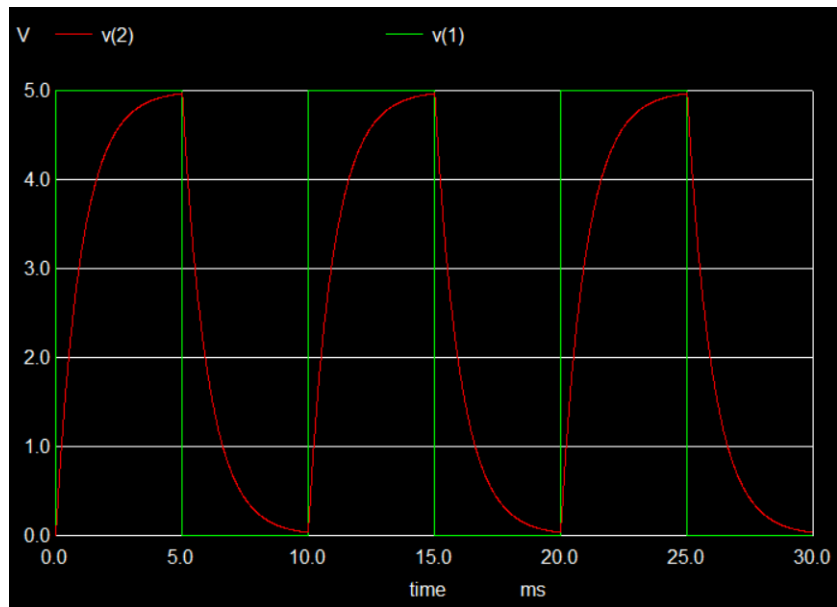

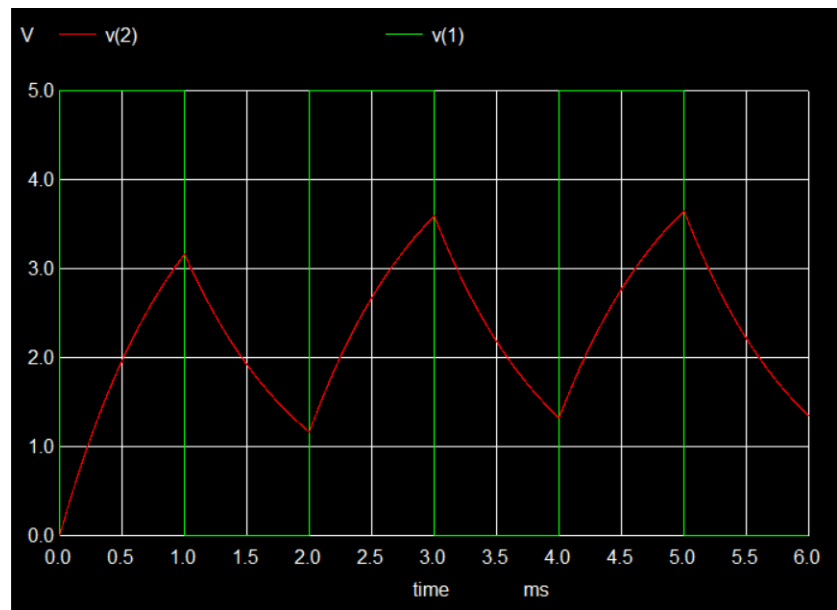
RC Integrator for $T = 5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



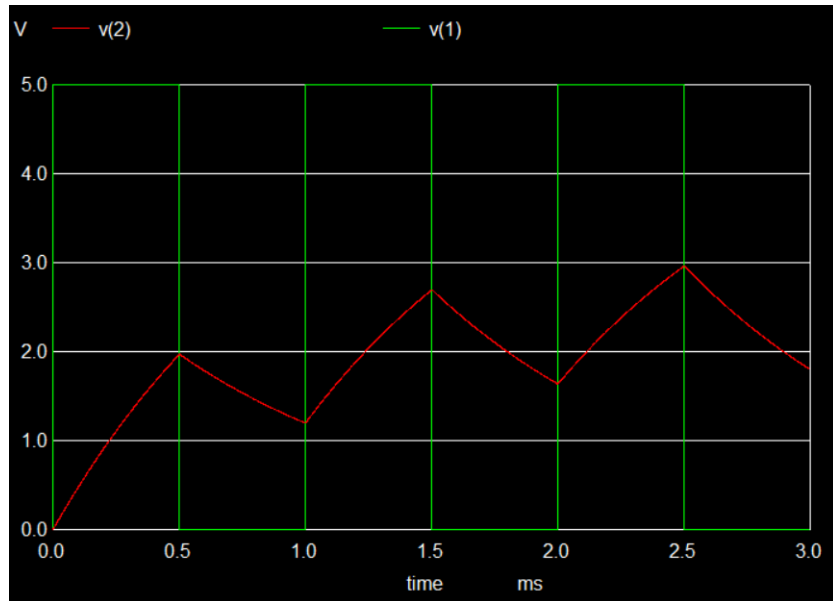
RC Integrator for $T = \tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



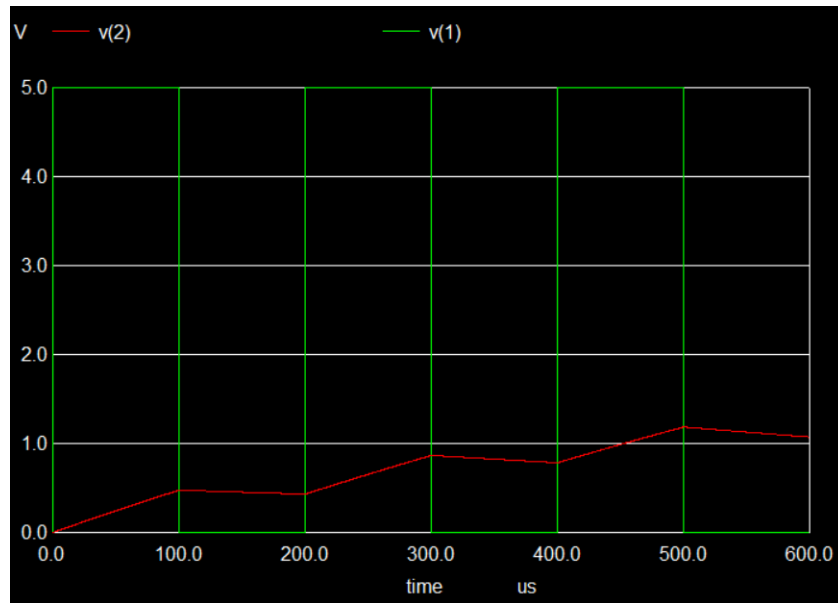
RC Integrator for $T = 0.5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



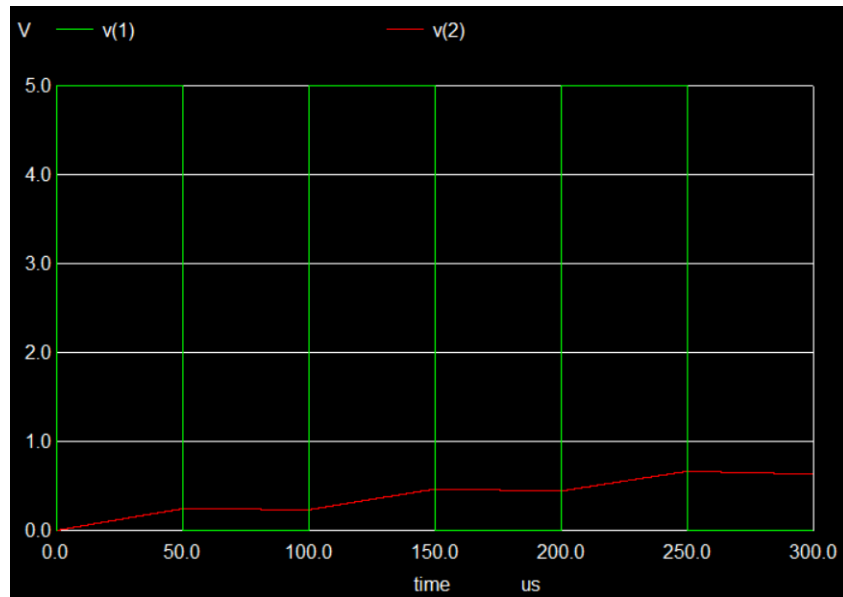
RC Integrator for $T = 0.1\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



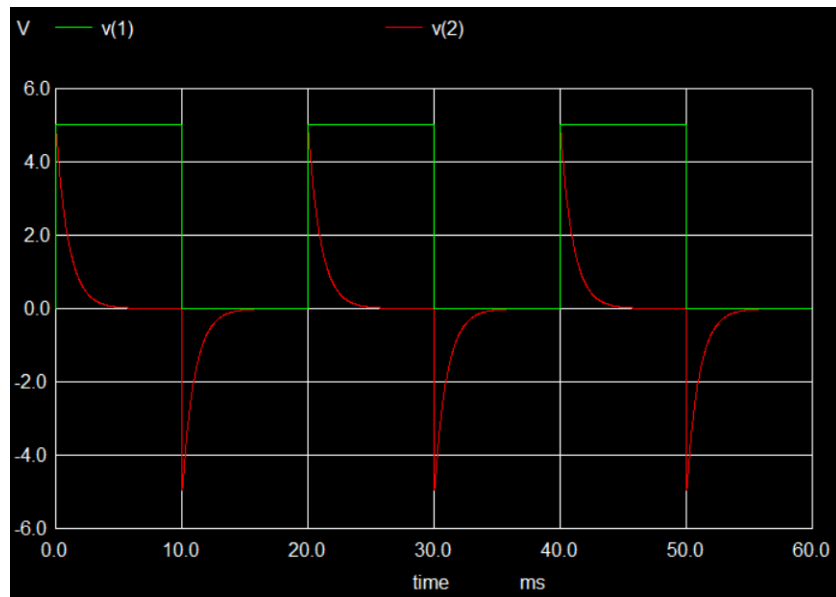
RC Integrator for $T = 0.01\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



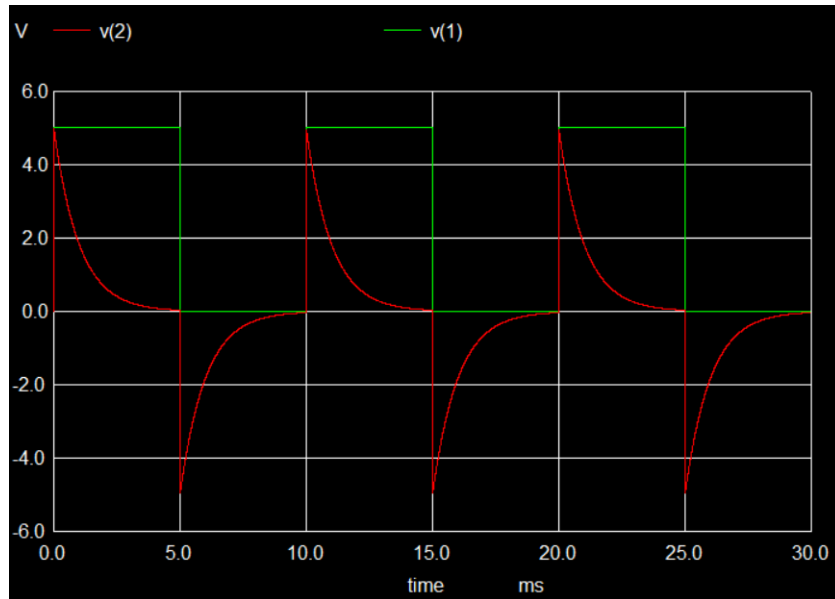
RC Differentiator for $T = 10\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



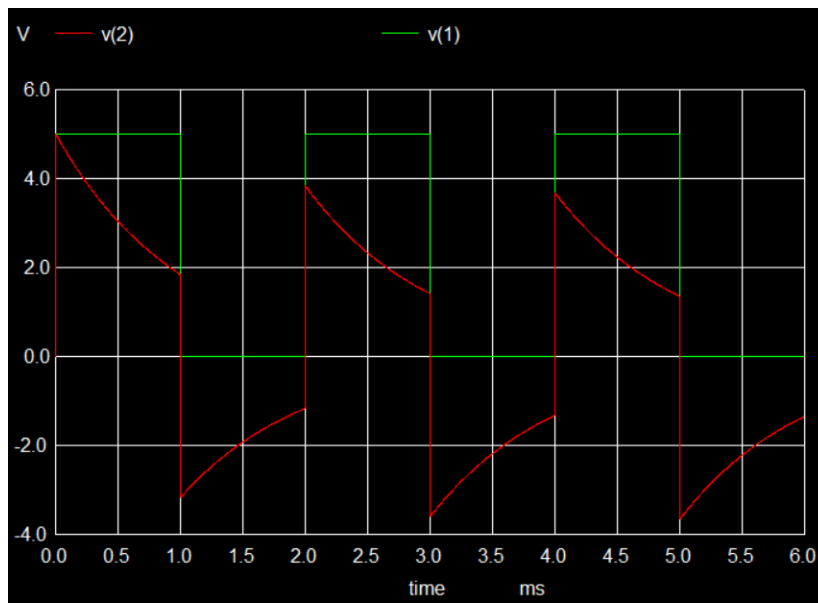
*RC Differentiator for $T = 5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}*



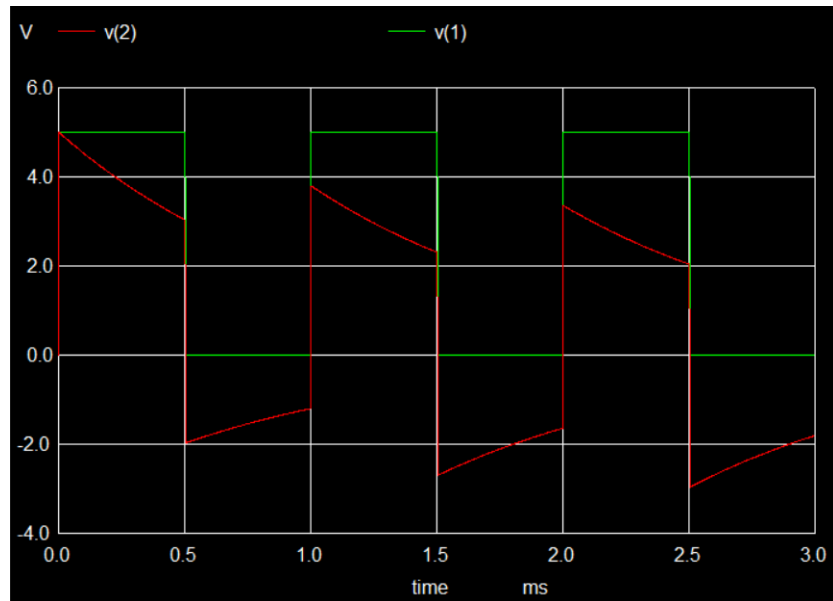
*RC Differentiator for $T = \tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}*



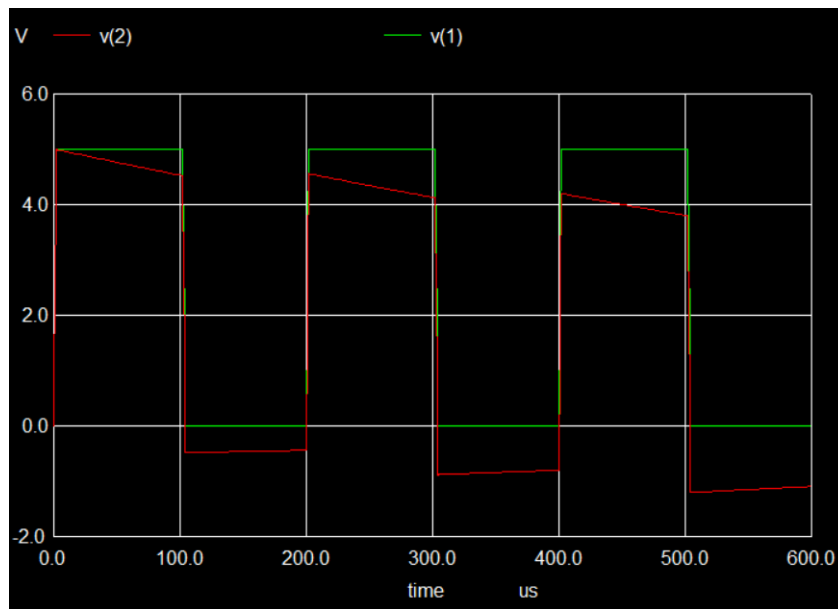
RC Differentiator for $T = 0.5\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



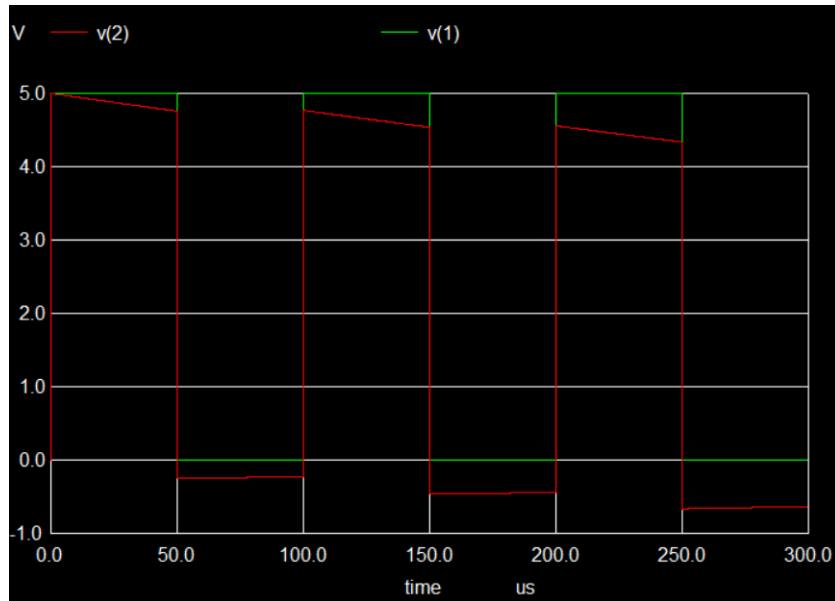
RC Differentiator for $T = 0.1\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}



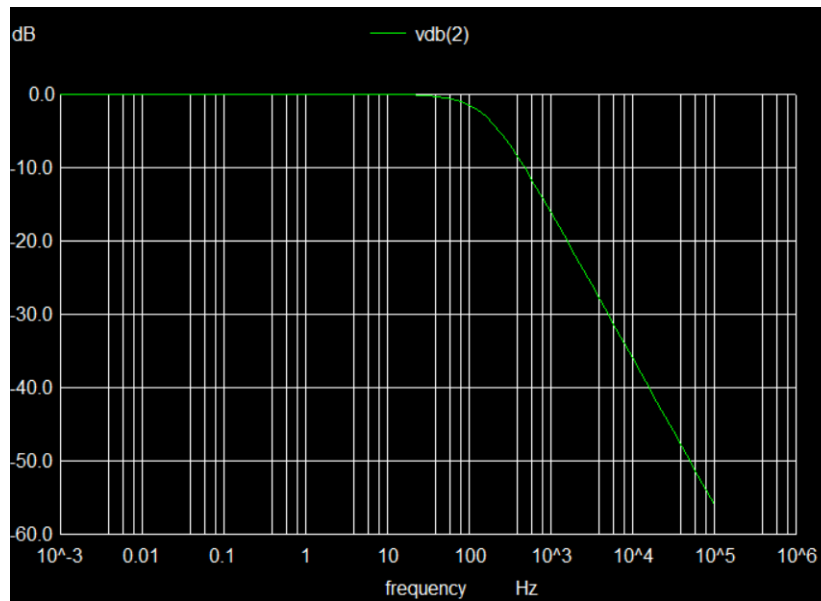
RC Differentiator for $T = 0.01\tau$
 $V(1)$: V_{in} , $V(2)$: V_{out}




Amplitude Bode Plot for RC Lowpass Filter
 $vdb(2)$: $20\log_{10}(|V_{out}|)$

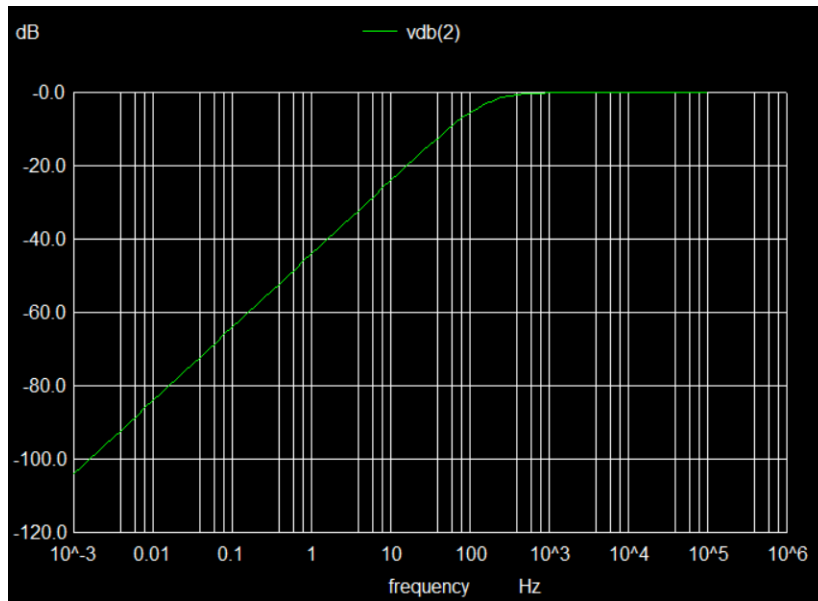

Amplitude Bode Plot for RC Highpass Filter
 $vdb(2): 20\log_{10}(|V_{out}|)$

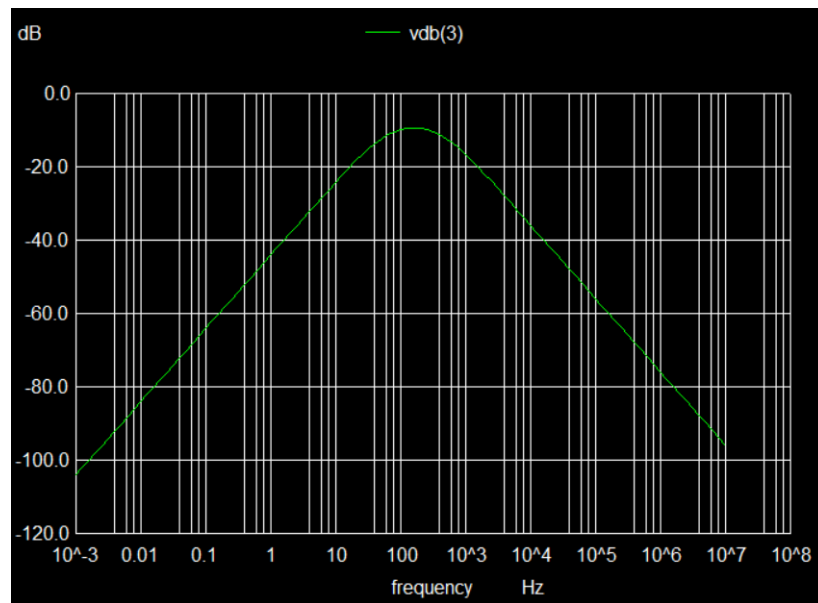

Amplitude Bode Plot for RC Bandpass Filter
 $vdb(3): 20\log_{10}(|V_{out}|)$

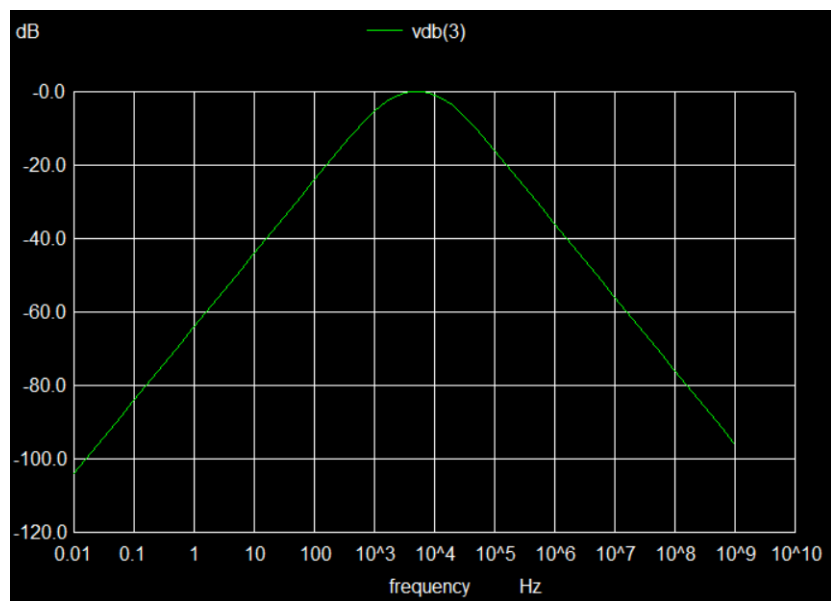

Amplitude Bode Plot for RLC Bandpass Filter
 $vdb(3): 20\log_{10}(|V_{out}|)$