

# EE230- Analog lab (Labwork-3)

## Spring Semester: Year 2021-22

January 22, 2022

---

### Instructions:

- Write your netlists and show the simulation results of each question to the evaluating TA during the lab session on Jan 27, 2022.
  - **No Additional time will be given.**
  - **You can refer:** NGSPICE tutorial, model files of op-amp "ua741.txt" and diode "1n914.txt" uploaded on the course moodle / MS Teams channel and your written netlists of previous experiments / homeworks.
- 

#### 1. Half-wave Precision Rectifier

- (a) Simulate the circuit "Improved half-wave rectifier-A" shown in figure [ 1] using Ngspice. Apply a sinusoidal input signal,  $V_i$  of  $10V_{pp}$  and  $1kHz$ . Plot  $V_o$ ,  $V_{o1}$  and  $V_i$  waveform on the same plot.

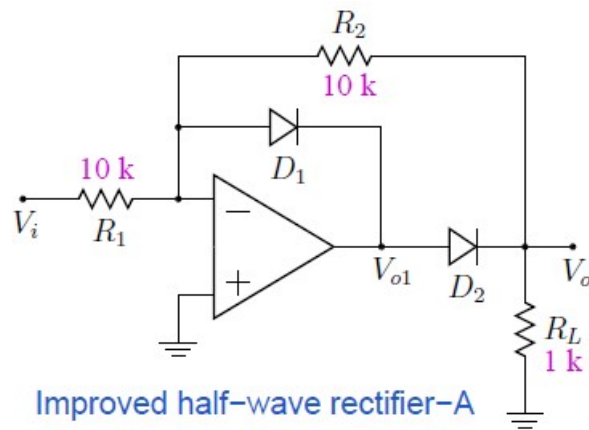


Figure 1: Improved Half Wave Rectifier-A Circuit

- (b) Simulate the circuit “Improved half-wave rectifier-B” shown in figure [ 2] using Ngspice. Apply a sinusoidal input signal,  $V_i$  of  $10V_{pp}$  and  $1kHz$ . Plot  $V_o$  ,  $V_{o1}$  and  $V_i$  waveform on the same plot.

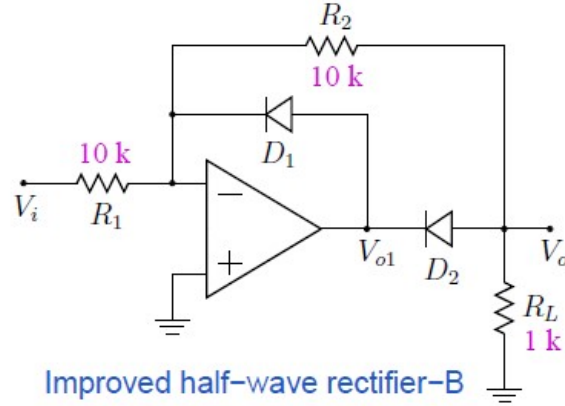


Figure 2: Improved Half Wave Rectifier-B Circuit

## 2. Full-wave Precision Rectifier

- (a) Use “Improved half-wave rectifier-B” as a sub-circuit and simulate the “Full-wave rectifier” circuit shown in figure [ 3] using Ngspice. Apply a sinusoidal input signal,  $V_i$  of  $10V_{pp}$  and  $1kHz$ . Plot  $V_o$  and  $V_i$  waveform on the same plot.

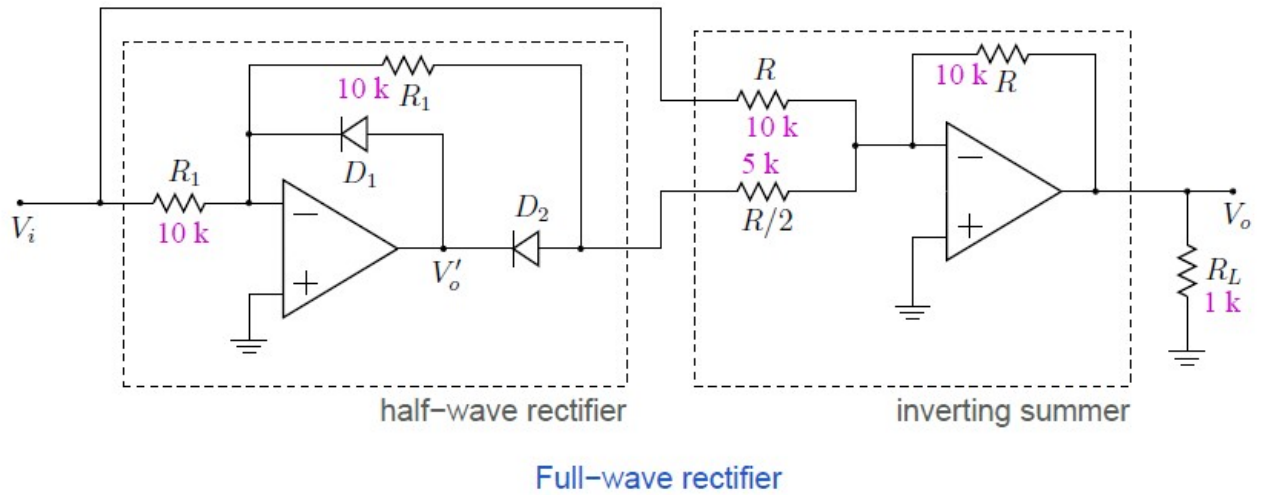


Figure 3: Full Wave Rectifier Circuit