

# EE230 Homework 1

## NGSPICE simulation of RC and RLC circuits

Name. Rohan Rajesh Kalbag, Roll. 20D170033


January 11, 2022

### 1 Overview of the experiment


#### 1.1 Aim of the experiment

To simulate RC Integrator, RC Differentiator, RC lowpass, RC highpass, RC bandpass and RLC bandpass circuits using NGSPICE.


#### 1.2 Circuit Diagrams

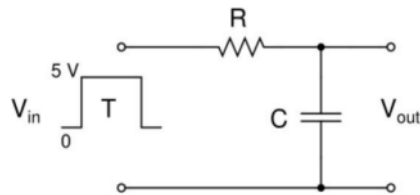


*RC Integrator Circuit*

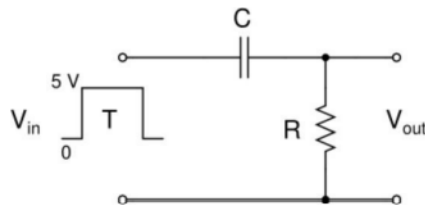


*RC Differentiator Circuit*

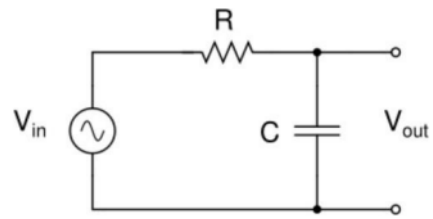


*RC Lowpass Filter Circuit*

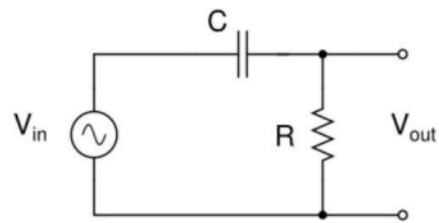

*RC Highpass Filter Circuit*

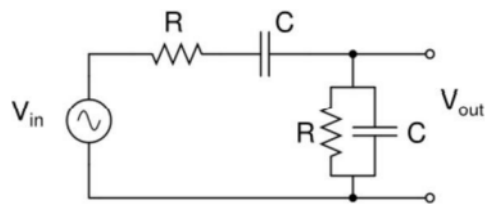

*RC Bandpass Filter Circuit*

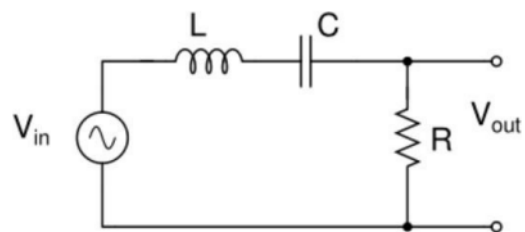

*RLC Bandpass Filter Circuit*

## 2 Simulation Code Snippets

### 2.1 B1 - RC Integrator

#### 2.1.1 $T = 10\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.01 0.02)
* Analysis Command
.tran 0.01m 0.06
.control
run
plot v(1) v(2)
.endc
.end
```

#### 2.1.2 $T = 5\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.005 0.01)
* Analysis Command
.tran 0.01m 0.03
.control
run
plot v(1) v(2)
.endc
.end
```

### 2.1.3 $T = \tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.001 0.002)
* Analysis Command
.tran 0.001m 0.006
.control
run
plot v(1) v(2)
.endc
.end
```

### 2.1.4 $T = 0.5\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.0005 0.001)
* Analysis Command
.tran 0.001m 0.003
.control
run
plot v(1) v(2)
.endc
.end
```

### 2.1.5 $T = 0.1\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.0001 0.0002)
* Analysis Command
.tran 0.0001m 0.0006
.control
run
plot v(1) v(2)
.endc
.end
```

### 2.1.6 $T = 0.05\tau$

```
RC Integrator
* Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 pulse(0 5 0 0 0 0.05m 0.1m)
* Analysis Command
.tran 0.01u 0.3m
.control
run
plot v(1) v(2)
.endc
.end
```

## 2.2 B2 - RC Differentiator

### 2.2.1 $T = 10\tau$

RC Differentiator

\* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 10m 20m)

\* Analysis Command

.tran 0.02m 60m

.control

run

plot v(1) v(2)

.endc

.end

### 2.2.2 $T = 5\tau$

RC Differentiator

\* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.005 0.01)

\* Analysis Command

.tran 0.002m 0.03

.control

run

plot v(1) v(2)

.endc

.end

### 2.2.3 $T = \tau$

RC Differentiator

\* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.001 0.002)

\* Analysis Command

.tran 0.002m 0.006

.control

run

plot v(1) v(2)

.endc

.end

### 2.2.4 $T = 0.5\tau$

RC Differentiator

\* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.5m 1m)

\* Analysis Command

.tran 0.002m 3m

.control

run

plot v(1) v(2)

.endc

.end

### 2.2.5 $T = 0.1\tau$

RC Differentiator

\* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.1m 0.2m)

\* Analysis Command

.tran 0.002m 0.6m

.control

run

plot v(1) v(2)

.endc

.end

### 2.2.6 $T = 0.05\tau$

RC Differentiator

\* Components

c1 1 2 0.1u

r1 2 0 10k

V1 1 0 pulse(0 5 0 0 0 0.05m 0.1m)

\* Analysis Command

.tran 0.0001m 0.3m

.control

run

plot v(1) v(2)

.endc

.end



## 2.3 B3 - RC Lowpass Filter

```
RC lowpass filter
*Components
r1 1 2 10k
c1 2 0 0.1u
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 1m 100k
.control
run
plot vdb(2)
.endc
.end
```

## 2.4 B4 - RC Highpass Filter

```
RC highpass filter
*Components
c1 1 2 0.1u
r1 2 0 10k
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 1m 100k
.control
run
plot vdb(2)
.endc
.end
```


## 2.5 B5 - RC Bandpass Filter

```
RC bandpass filter
*Components
r1 1 2 10k
c1 2 3 0.1u
r2 3 0 10k
c2 3 0 0.1u
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 1m 10Meg
.control
run
plot vdb(3)
.endc
.end
```


## 2.6 B5 - RLC Bandpass Filter

```
RLC bandpass filter
*Components
l1 1 2 10m
c1 2 3 0.1u
r2 3 0 1k
V1 1 0 dc 0 ac 1 $ac analysis
*Analysis Command
.ac dec 10 10m 1000Meg
.control
run
plot vdb(3)
.endc
.end
```


## 2.7 Simulation Plots

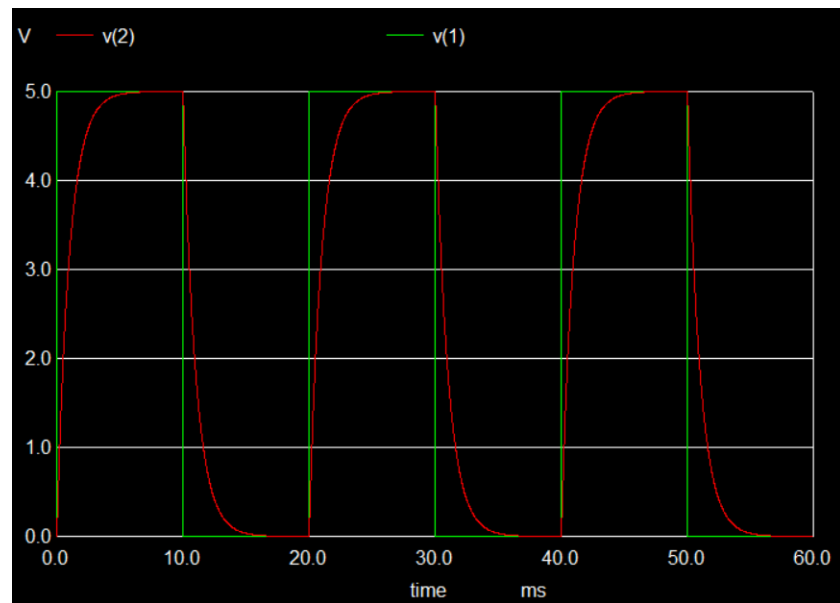

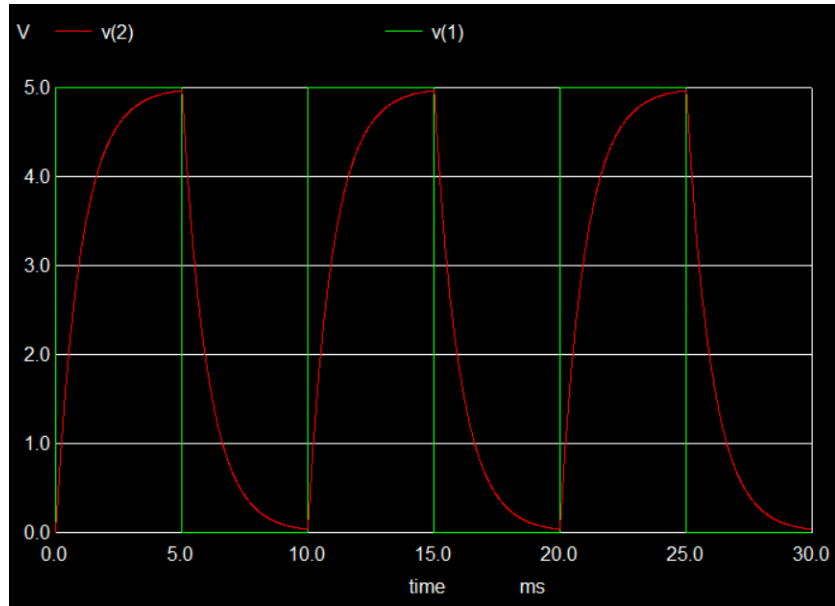
*RC Integrator for  $T = 10\tau$*   
*V(1):  $V_{in}$ , V(2):  $V_{out}$*



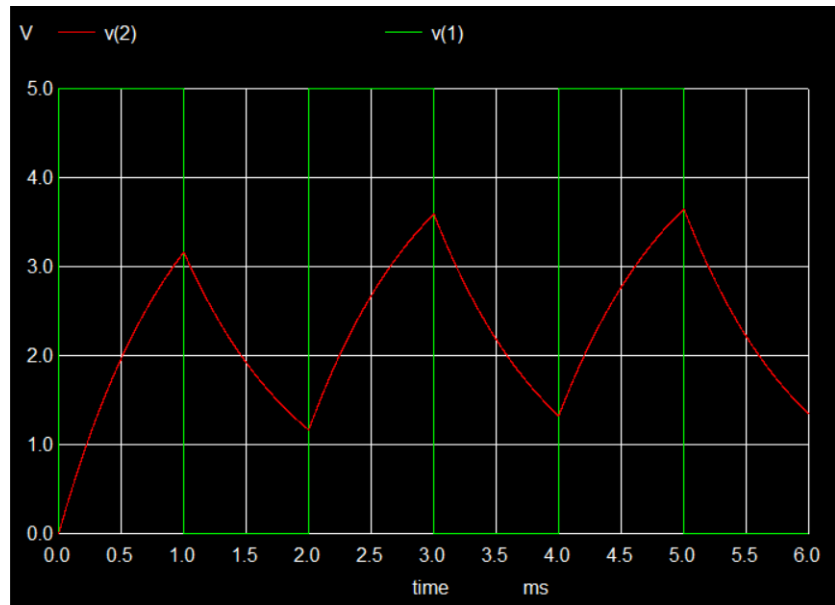
*RC Integrator for  $T = 5\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*



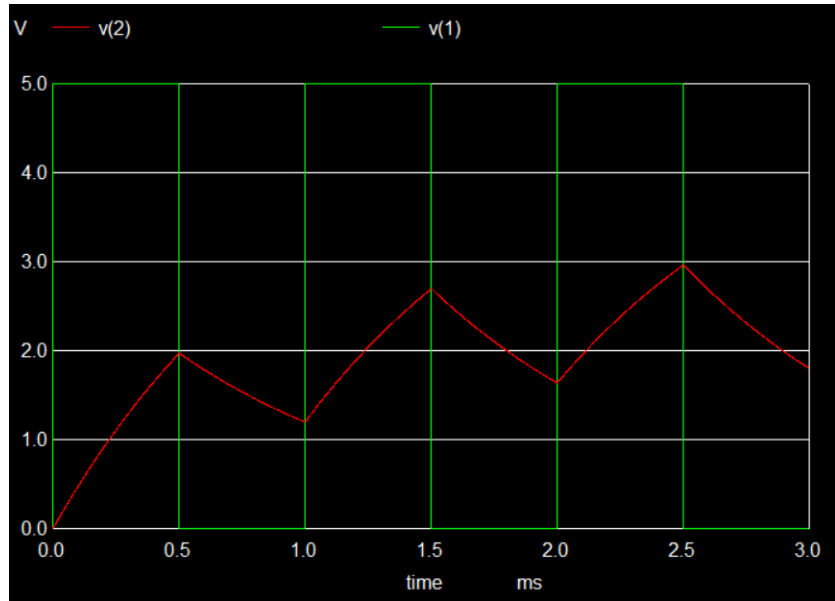
*RC Integrator for  $T = \tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*



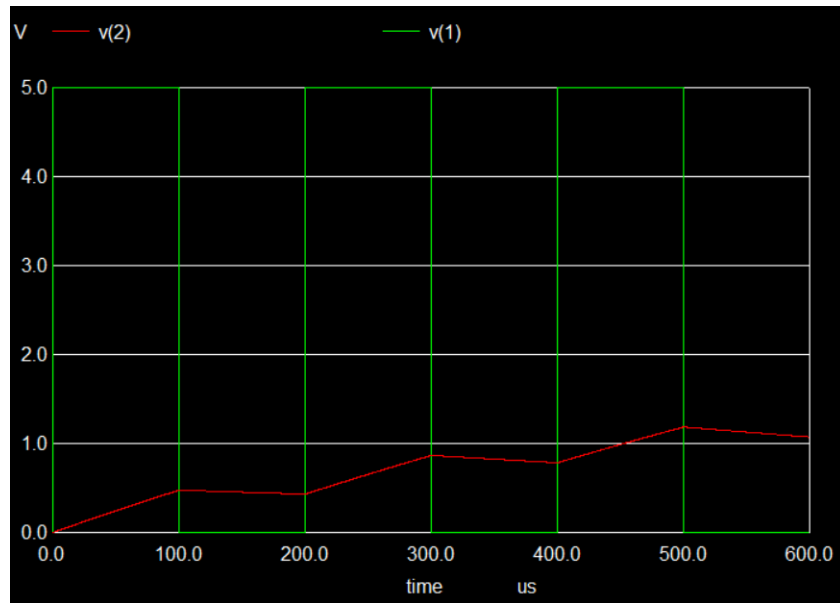
*RC Integrator for  $T = 0.5\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*



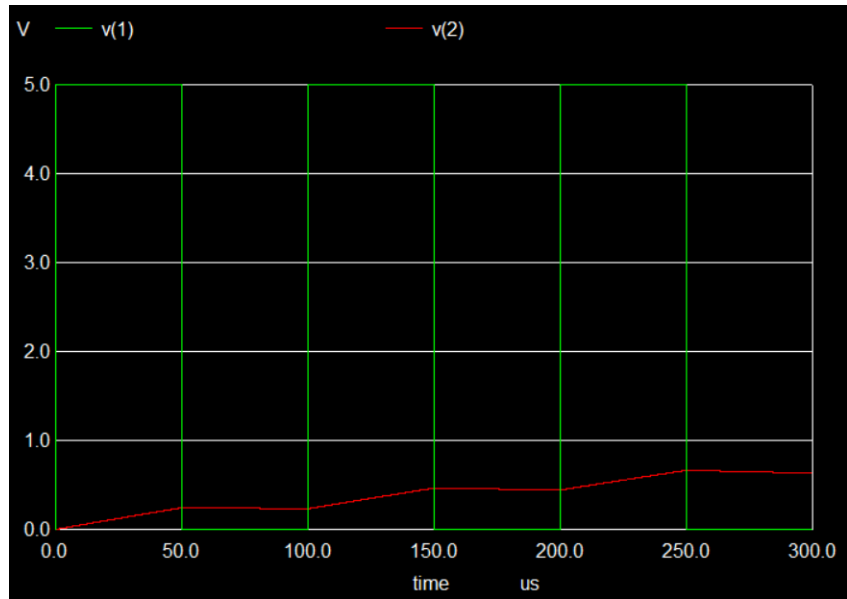
*RC Integrator for  $T = 0.1\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*



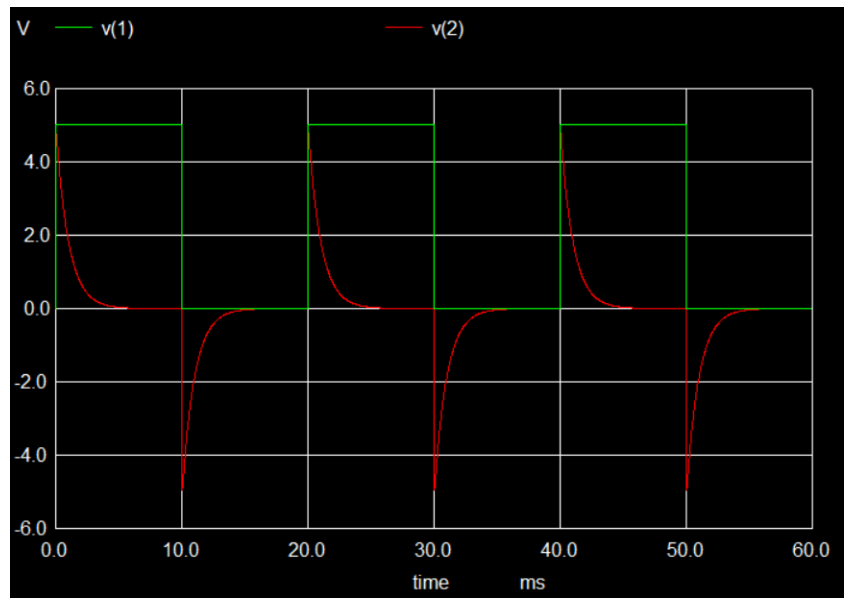
*RC Integrator for  $T = 0.01\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*



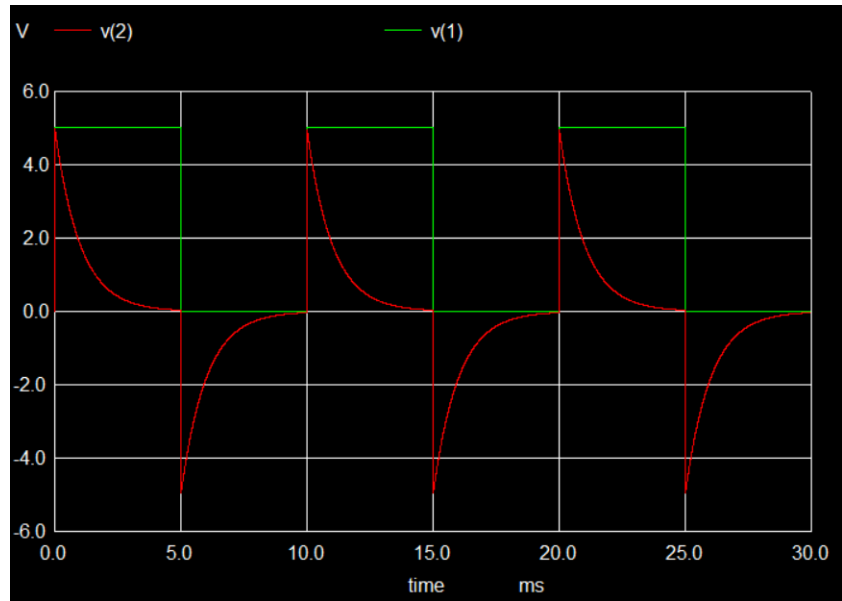
*RC Differentiator for  $T = 10\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*



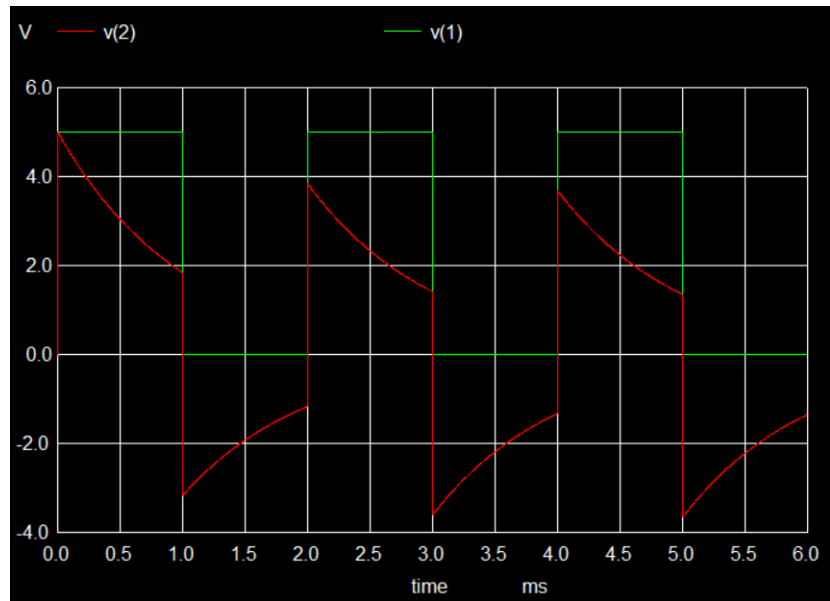
*RC Differentiator for  $T = 5\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*



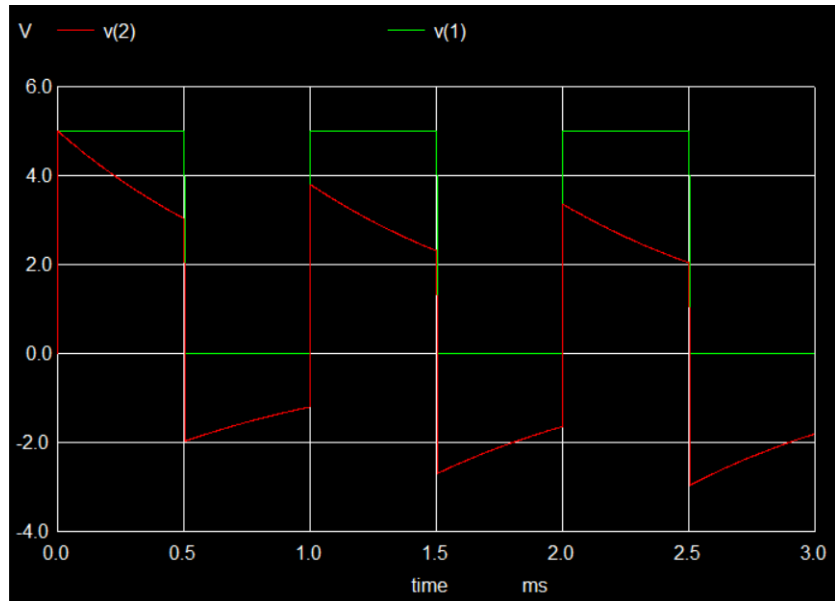*RC Differentiator for  $T = \tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*




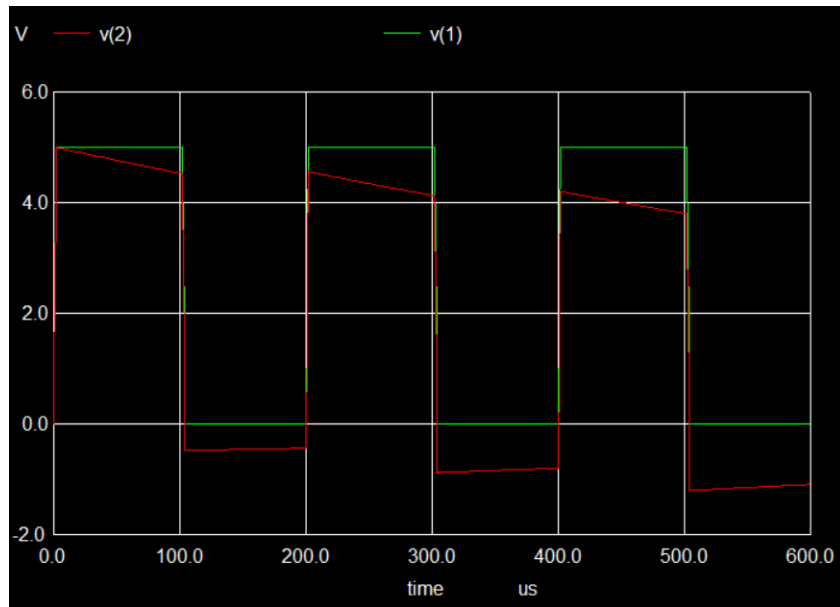*RC Differentiator for  $T = 0.5\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*




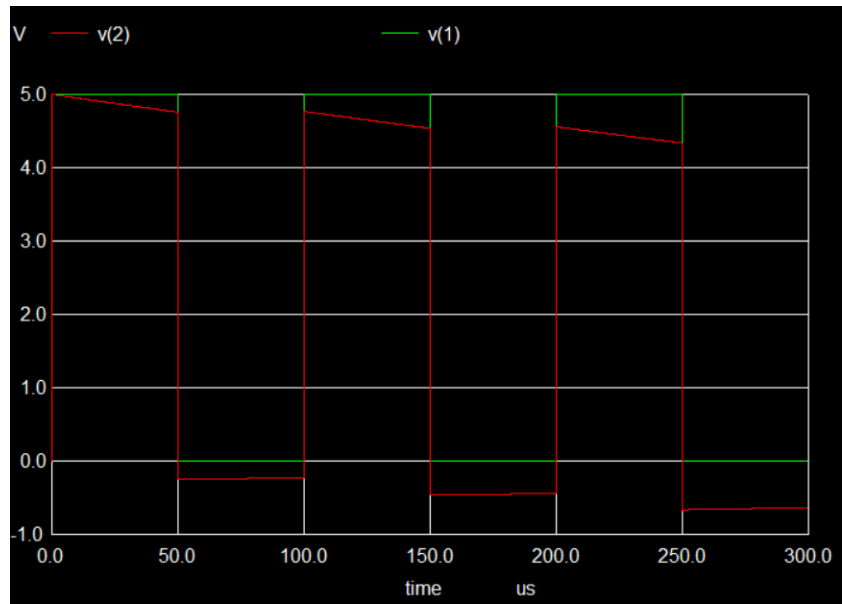*RC Differentiator for  $T = 0.1\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*






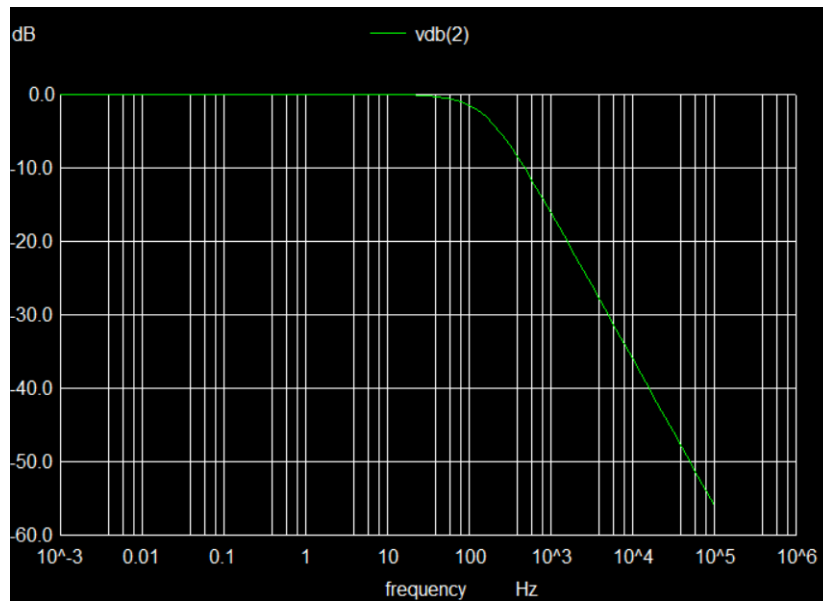
*RC Differentiator for  $T = 0.01\tau$*   
 *$V(1)$ :  $V_{in}$ ,  $V(2)$ :  $V_{out}$*




*Amplitude Bode Plot for RC Lowpass Filter*  
 *$vdb(2)$ :  $20\log_{10}(|V_{out}|)$*

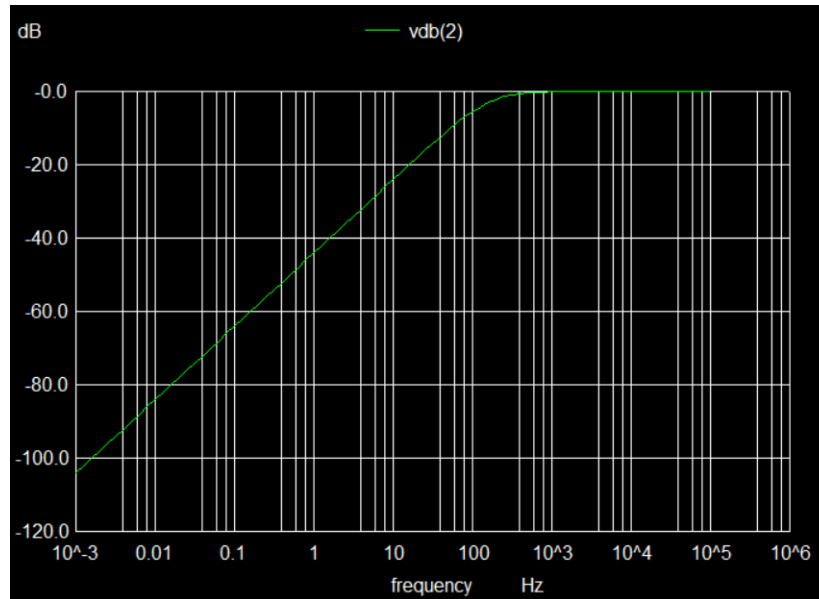

*Amplitude Bode Plot for RC Highpass Filter*  
 $vdb(2): 20\log_{10}(|V_{out}|)$

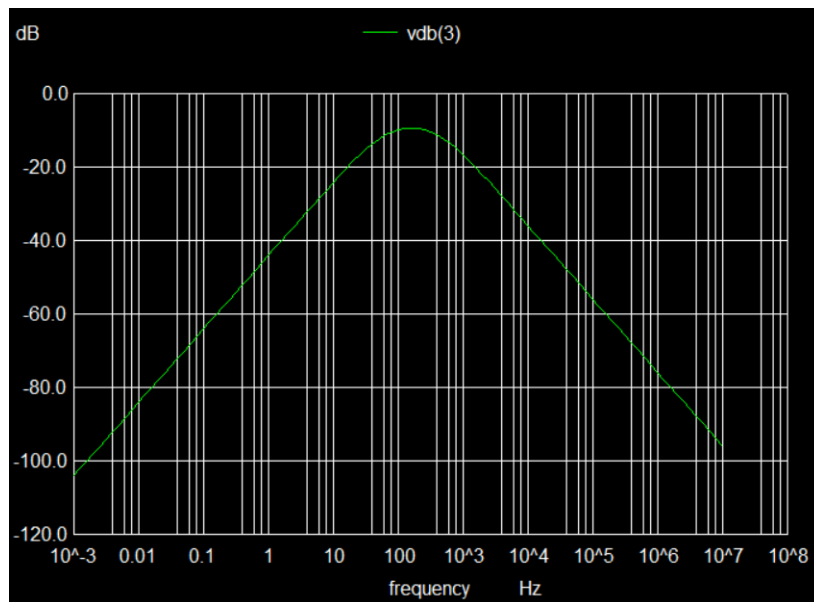

*Amplitude Bode Plot for RC Bandpass Filter*  
 $vdb(3): 20\log_{10}(|V_{out}|)$

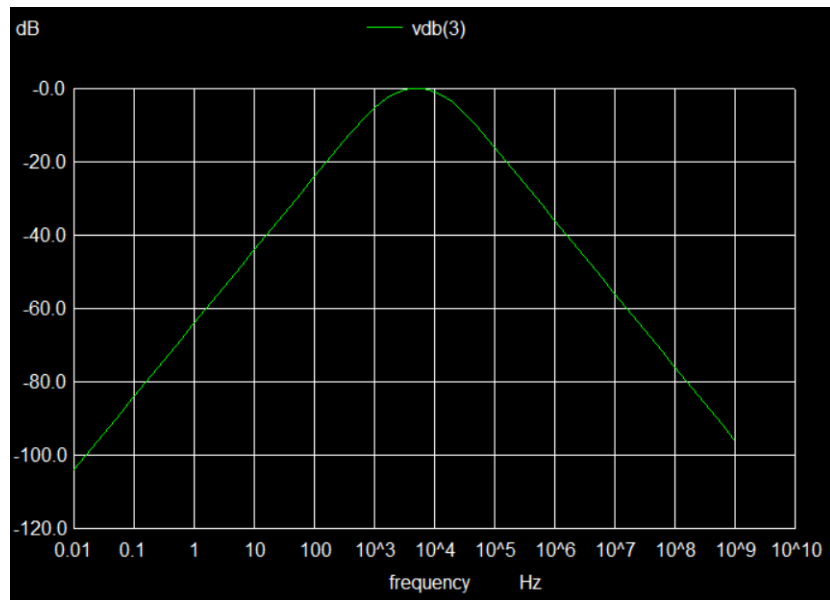

*Amplitude Bode Plot for RLC Bandpass Filter*  
*vdb(3):  $20\log_{10}(|V_{out}|)$*